

- Find the sinusoids corresponding to these phasors:
 - $V = -25 \angle 40^\circ \text{ V}$
 - $I = j(12 - j5) \text{ A}$
 - $I = -3 + 4j \text{ A}$
 - $V = j8e^{-j20^\circ} \text{ V}$
- Calculate the phase angle between $v_1 = -10 \cos(\omega t + 50^\circ)$ and $v_2 = 12 \sin(\omega t - 10^\circ)$. State which sinusoid is leading.
- Evaluate the following complex number and write the expression in rectangular form and phasor form both
 - $(40 \angle 50^\circ + 20 \angle -30^\circ)^{\frac{1}{2}}$
 - $\frac{10 \angle -30^\circ + (3 - j4)}{(2 + j4)(3 - j5)^*}$ (Where * represents conjugate)
 - $[(5 + 2j)(1 + 4j) - 5 \angle 60^\circ]^*$ (Where * represents conjugate)
 - $\frac{10 + 5j + 3 \angle 40^\circ}{-3 + j4} + 10 \angle 30^\circ + j5$
- Determine the input impedance of the circuit in Fig. 1 at $\omega = 10 \text{ rad/s}$.

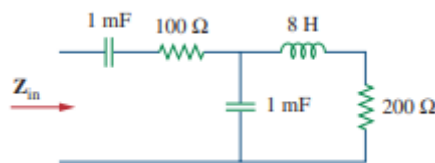


Fig. 1

- Calculate v_0 in the circuit of Fig. 2.

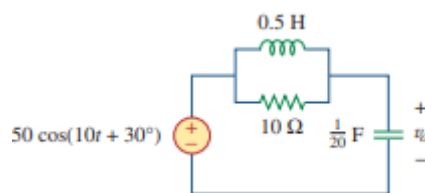


Fig. 2

- Find v_1 and v_2 in the given circuit as in Fig. 3.

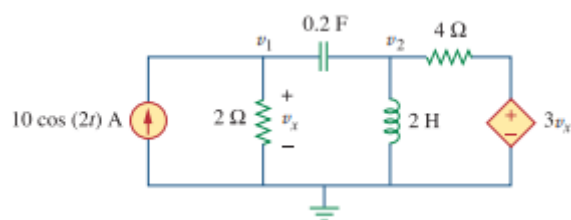


Fig. 3

7. Find the Thevenin equivalent across the terminal a-b as shown in Fig. 4.

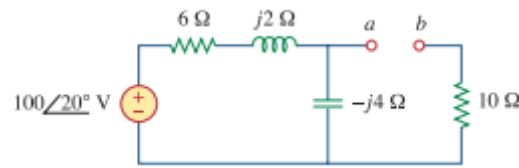


Fig. 4

8. Obtain current I_0 in Fig. 5 using Norton theorem.

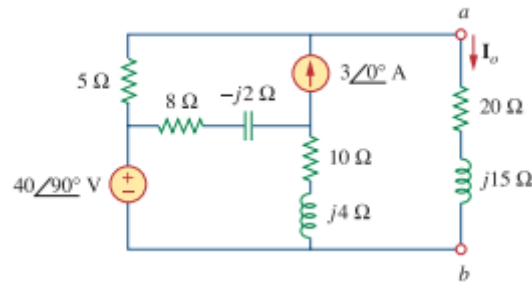


Fig. 5

9. Calculate the instantaneous power and average power for the given voltage and current expressions:

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V}$$

$$i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

10. For the circuit shown in Fig. 6, find the load impedance that absorbs the maximum active power. Calculate that maximum active power.

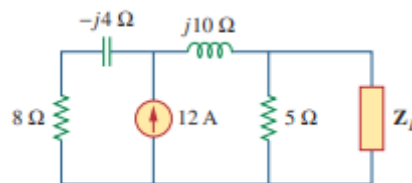


Fig. 6

11. Obtain the power factor and the apparent power of a load whose impedance is $Z = 60 + j40 \Omega$ when the applied voltage is $v(t) = 320 \cos(377t + 10^\circ) \text{ V}$.

12. For a load, $V_{rms} = 110 \angle 85^\circ \text{ V}$, $I_{rms} = 0.4 \angle 15^\circ \text{ A}$. Determine: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

13. Find the value of parallel capacitance needed to correct a load of 140 kVAR at 0.85 lagging pf to unity pf. Assume that the load is supplied by a 110 V (rms), 60-Hz line.