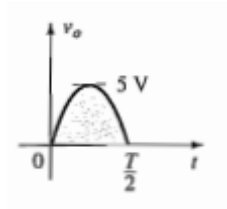


Assignment 3 Answer Key

1. $V_0 = 12\text{ V}$, LED will turn ON.

2. $V_0 = 0.7\text{ V}$, AND Gate


3.




4. $23.76 \leq V_i \leq 36.87\text{ Volts}$

5. $V_{01} = 4\text{ V}$, $V_{02} = 10\text{ V}$, $I_R = 20\text{ mA}$, $P_s = 800\text{ mW}$, $P_{LED} = 80\text{ mW}$,
 $P_Z = 120\text{ mW}$

6.

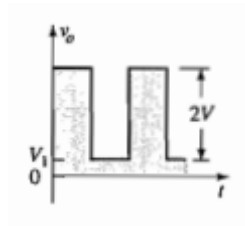

7.

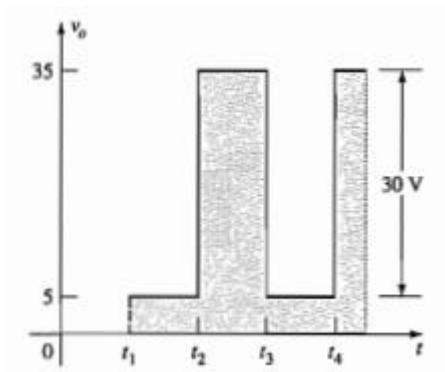

8. $V_0 = -(10V_1 + 33V_2)\text{ Volts} = -[0.5 \sin(1000t) + 0.33 \sin(3000t)]\text{ Volts}$

9. $V_0 = 0.729 \text{ V}$

10. $-3.8 \text{ V}, -1.425 \text{ mA}$.

11. $0.8 \text{ }\mu\text{A}$ to $1 \text{ }\mu\text{A}$

12. 7 Volt

13. $V_0 = -20(V_2 - V_1)$

14. $V_0 = 21(V_1 - V_2)$