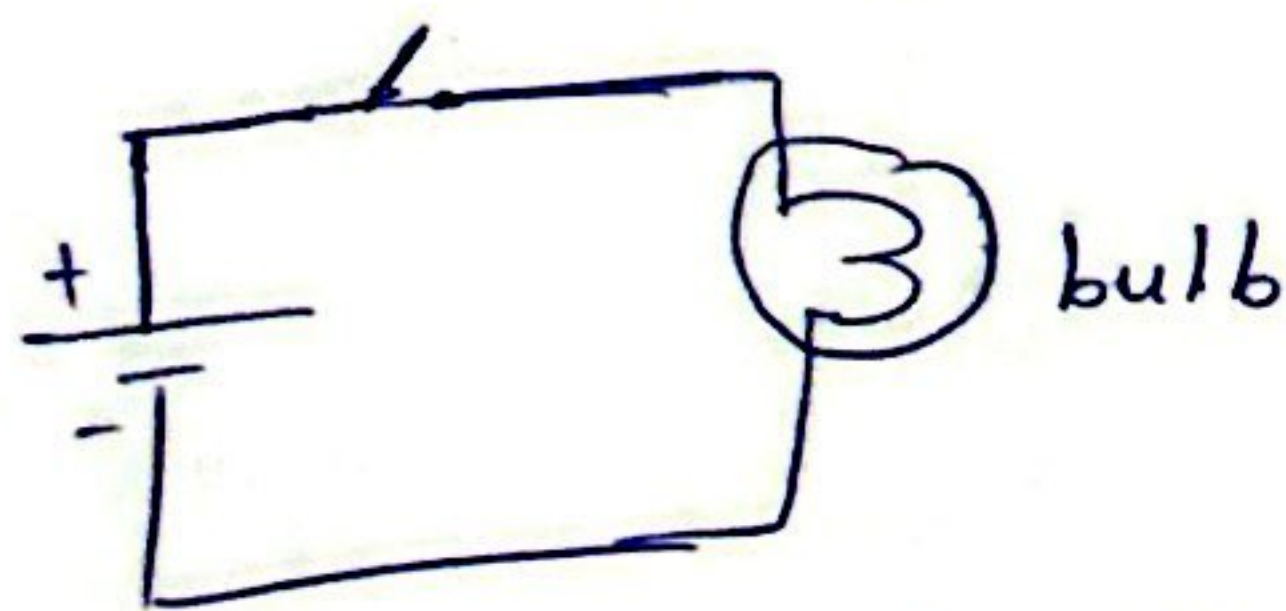


①

ELL 101

- What comes to mind when you think 'electrical engineering'?
- Name a device/gadget without which you can't live
- Name a technology without which you can't live
- All these devices/tech have circuits in them
open a mobile charger & show
- In this course, we learn about these circuits
↓
circulation such as blood in body; water



Electricity is everywhere around us: Atoms, molecules, nervous system

- like air of modern times
- sustainability ↔ electrification
[transportation, cooking, teaching]
- other components of elec eng.
 - control
 - communication
 - power
 - electronics
 -

Basic Concepts

- 1.) Charge (Q): most basic quant. in elec. circuit
elec. prop. of atomic particles measured in Coulombs (C)

$$1 \text{ elect.} = -1.602 \times 10^{-19} \text{ C}$$

- 2.) Current (I):

rate of change of charge, meas. in Amp.


$$i = dq/dt$$

$$1 \text{ Amp} = 1 \text{ coulomb/sec.}$$


$$Q = \int_{t_0}^t i \, dt$$

DC & AC current


- 3.) Voltage

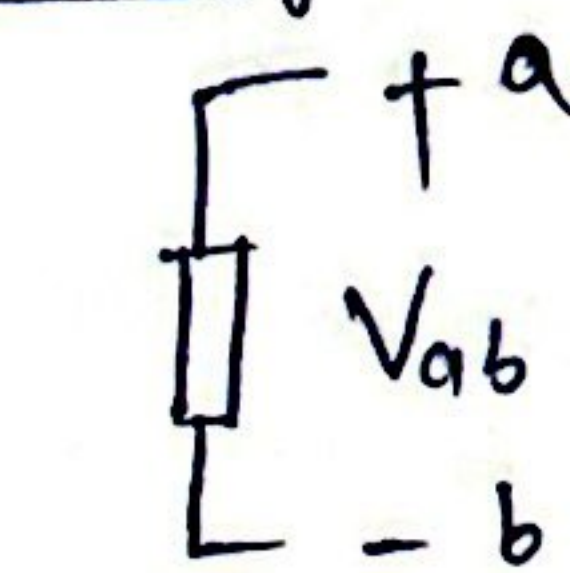

$$V_{ab} = -V_{ba}$$

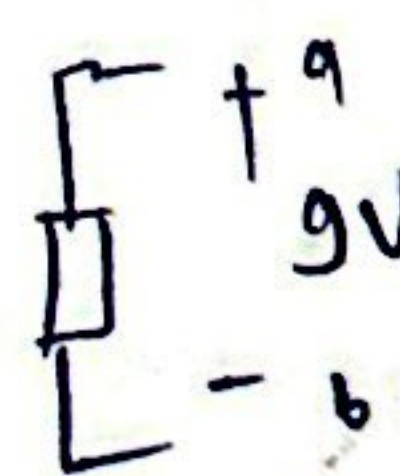

$$V_{ab} = 9V$$

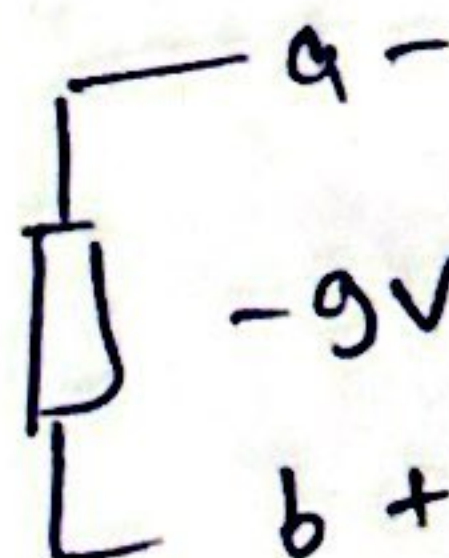

$$V_{ba} = -9V$$

Voltage (potential diff) is the energy required to move a unit charge from a ref. point ^(b) to another point ^(a), meas. in volts

$$V_{ab} = dw/dq$$

$$1 \text{ Volt} = 1 \text{ J/coulomb}$$


- 4.) Power: time rate of change in energy absorption or expansion (W)

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = V i$$

- 5.) Energy: Energy supplied or absorbed by an element from t_0 to t

$$W = \int_{t_0}^t P \, dt = \int_{t_0}^t V i \, dt$$

② $1 \text{ wh} = 3600 \text{ Joules}$

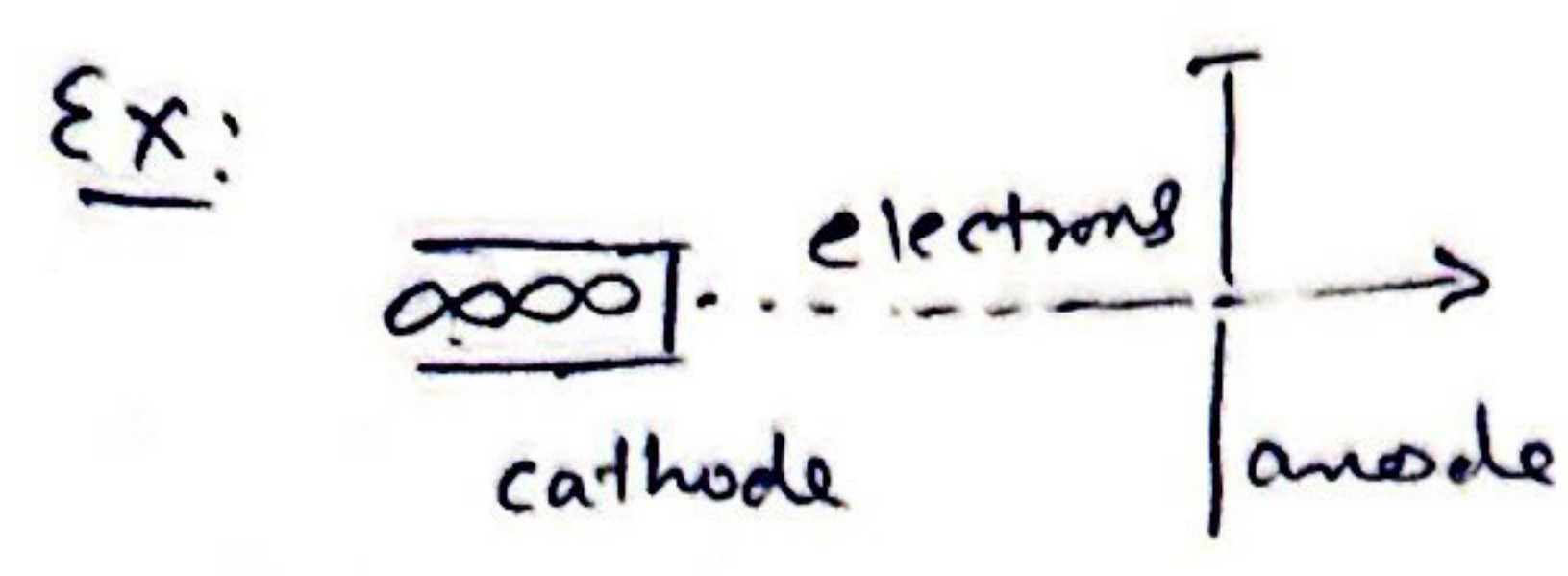


Calculate the power supplied to a beam of 50 million billion electrons per second through a potential diff of 20,000 volts.


$i = 1.6 \times 10^{-19} \times 50 \times 10^6 \times 10^9 = 0.008 \text{ A}$
 $P = V i = 2 \times 10^4 \times 8 \times 10^{-3} = 160 \text{ W}$

Basic Circuit Elements

1) Source


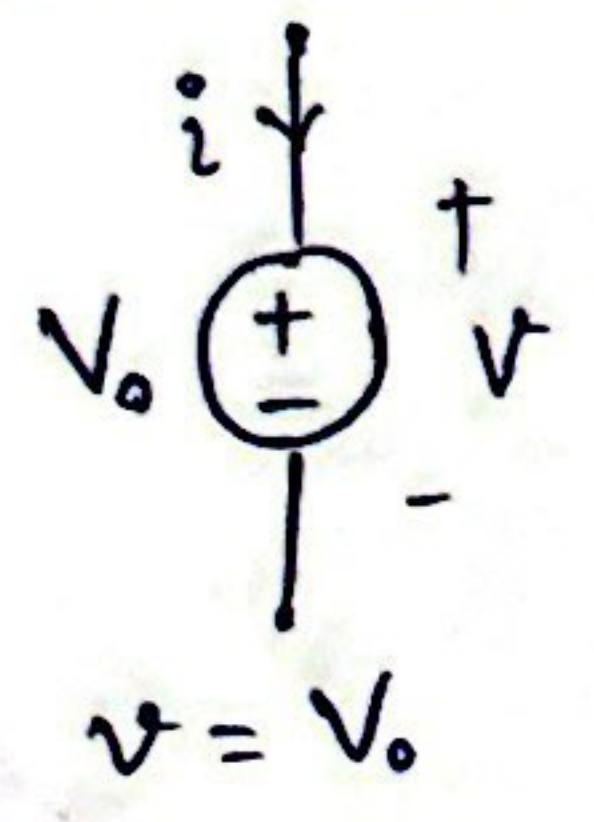


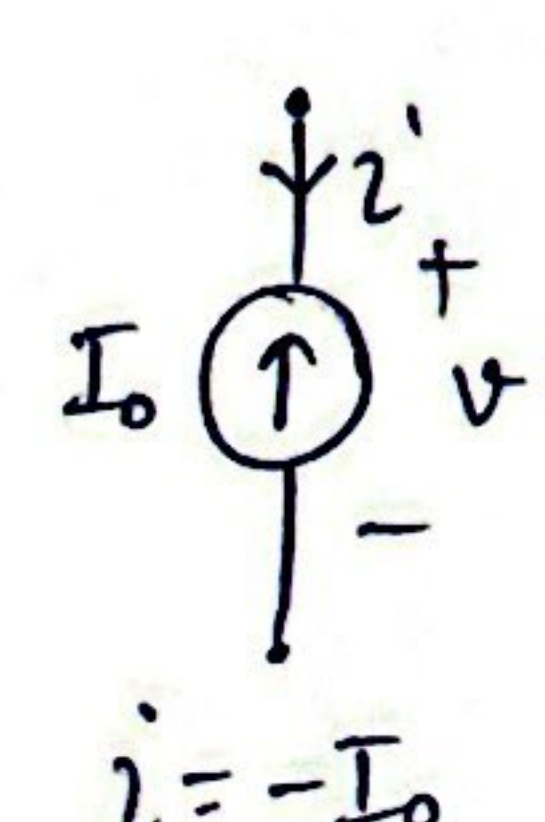$v = V_0$
 ideal voltage source
 independent of i ,
 or load connected




$i = -I_0$
 ideal current source
 independent of v
 or load connected

⇒ but practically, no ideal sources

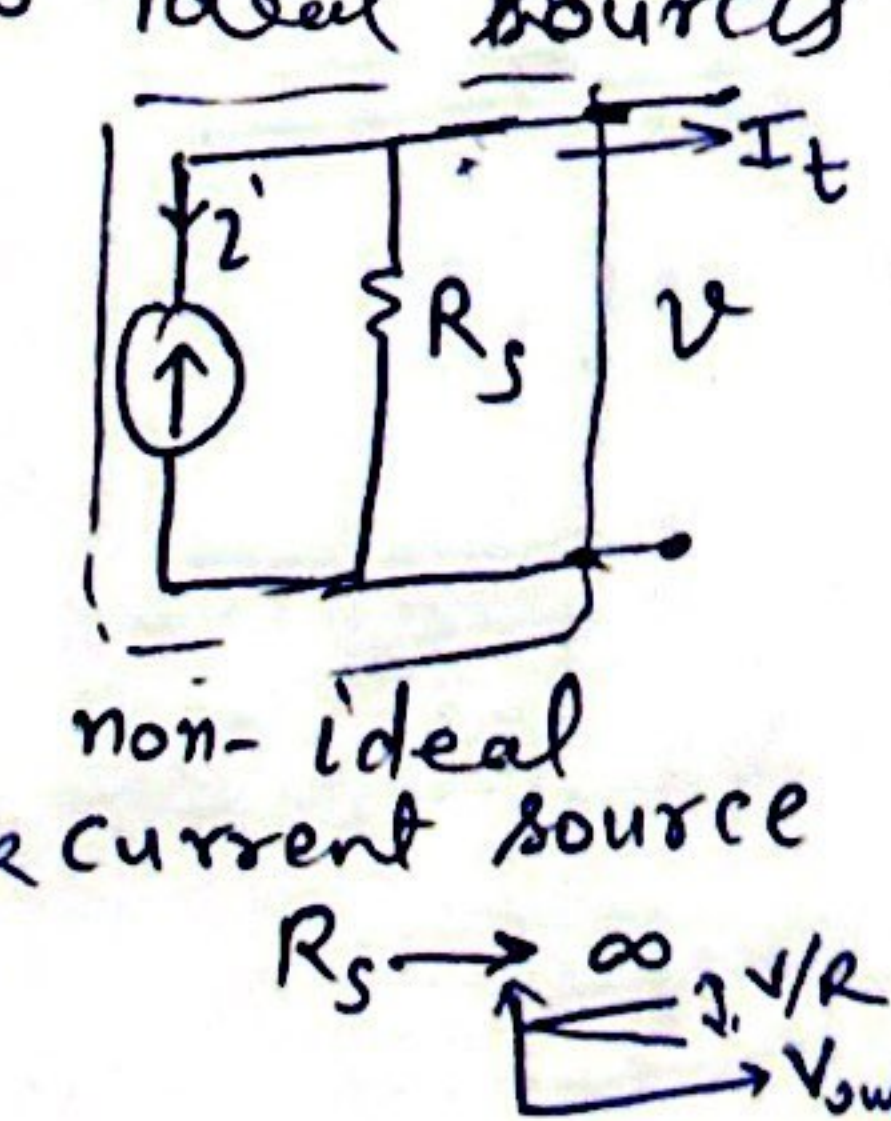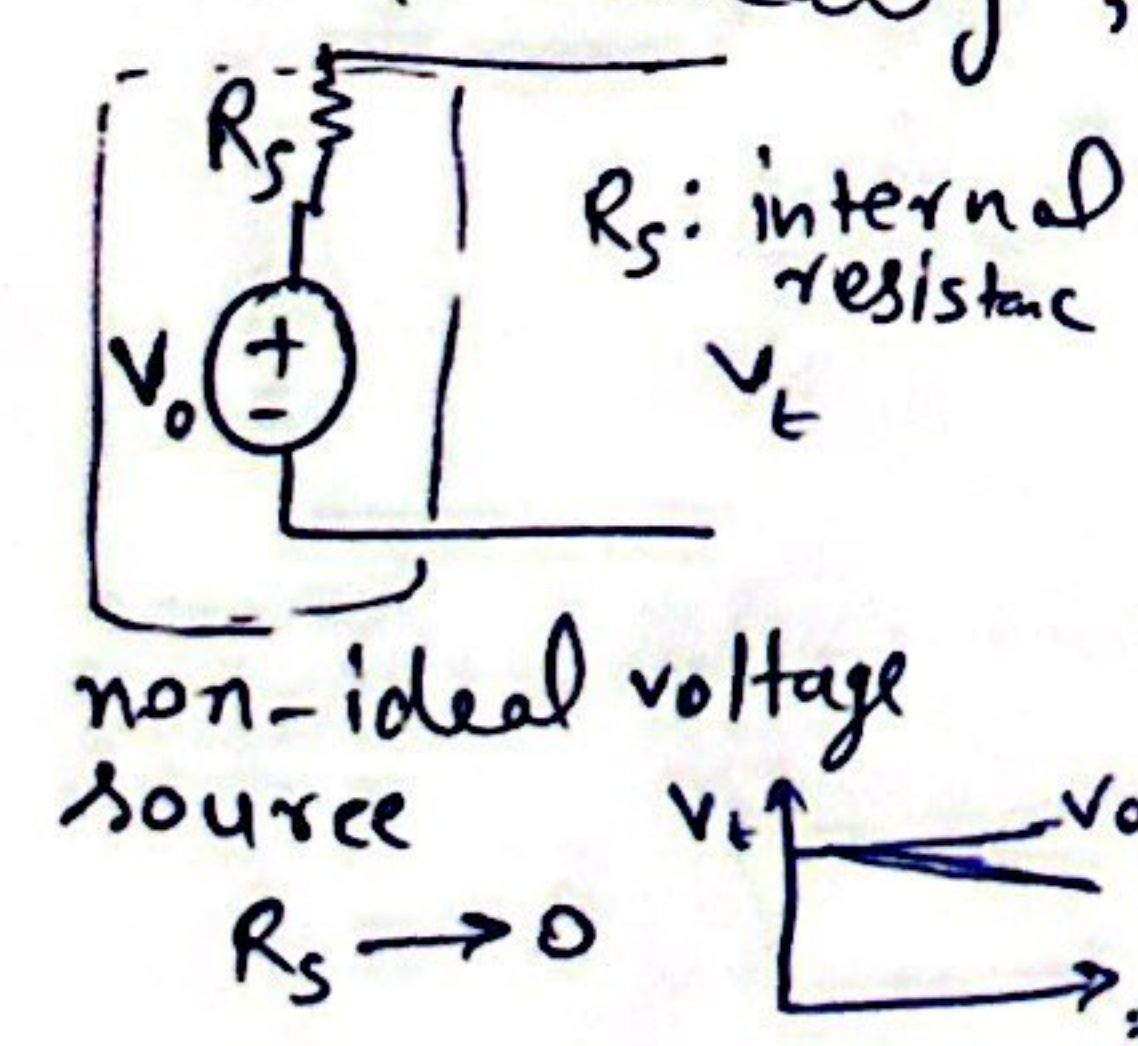


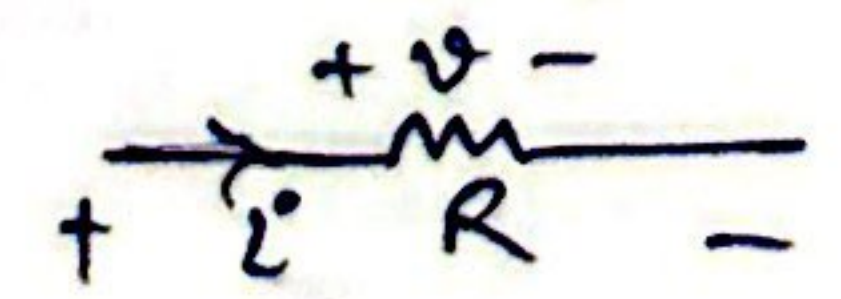2) Resistance: R of an material denotes it's ability to resist the flow of electric current, measured in ohms (Ω)



$V = iR$



$R = \frac{\rho l}{A}$

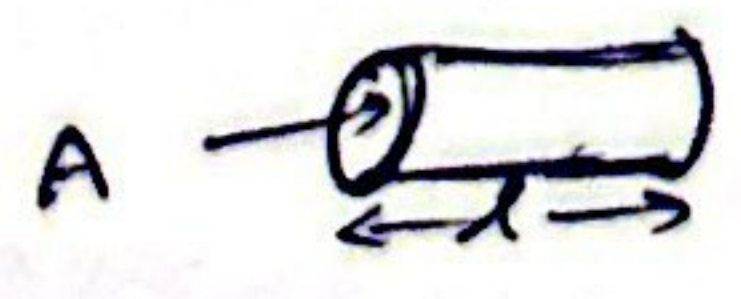


show slide 24-25 (R of common materials)
 ⇒ conductance: $G = \frac{1}{R}$ mho or Siemens (S)

⇒ Power dissipated by Resistor in heat
 $P = V i = i^2 R = V^2 / R$
 (irreversible)

⇒ Series & Parallel connection of R

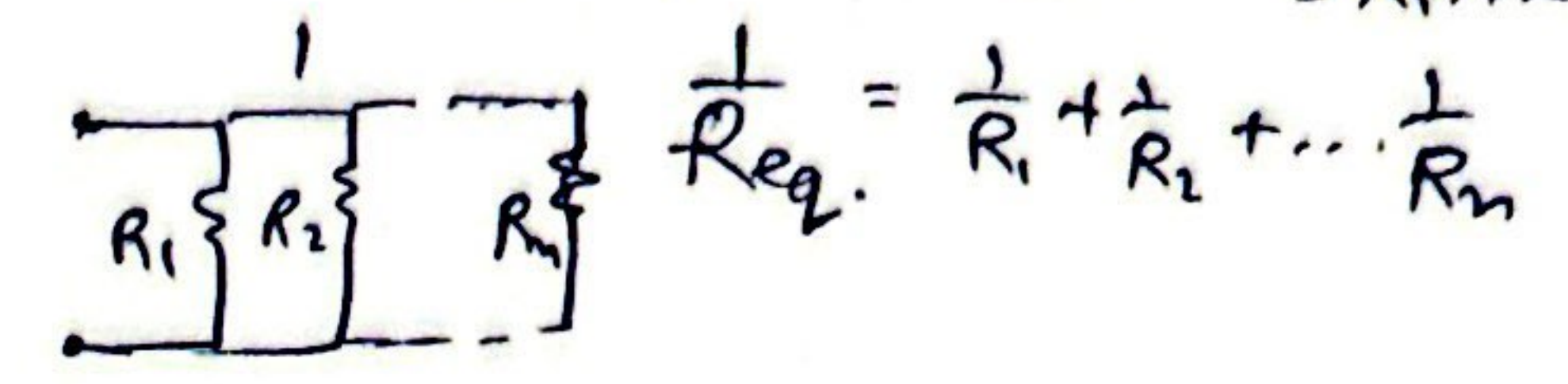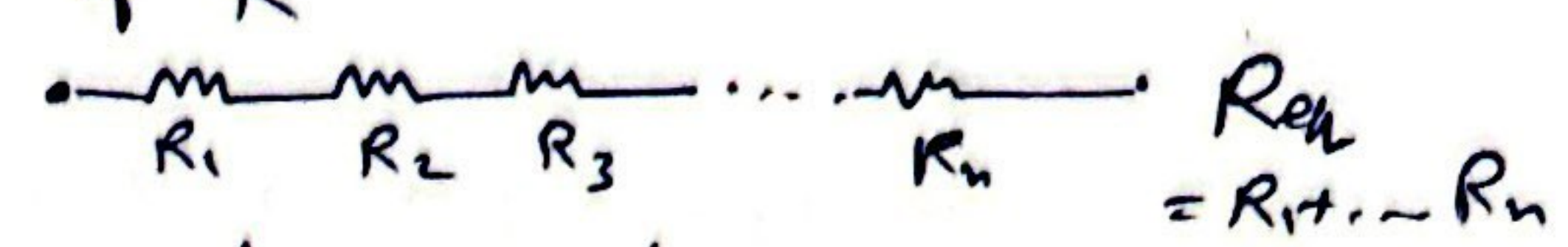

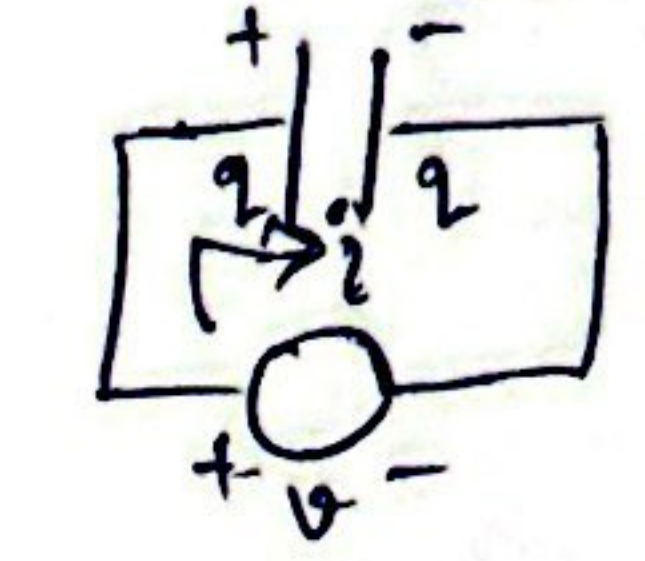3) Capacitor (C): two conducting plates, separated by an insulator




$q = C v$
 $dq/dt = C dv/dt$
 $i = C dv/dt$

ability to store energy in stationary charges or electric field

⇒ Energy stored: $E = \int_{t_0}^t V i dt = C \int_{v(t_0)}^{v(t)} v dv = \frac{1}{2} C v^2$

⇒ an abrupt change in voltage requires infinite current ⇒ Voltage can not change abruptly

⇒ non ideal capacitor

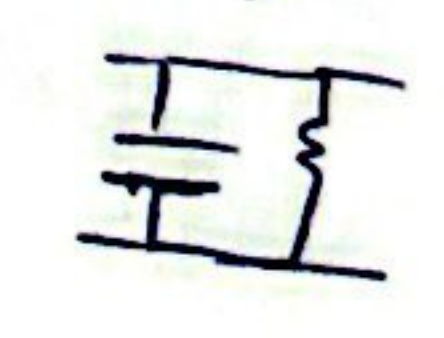


⇒ Cap in series


$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$

⇒ Cap in parallel

$C_{eq} = C_1 + C_2 + \dots$

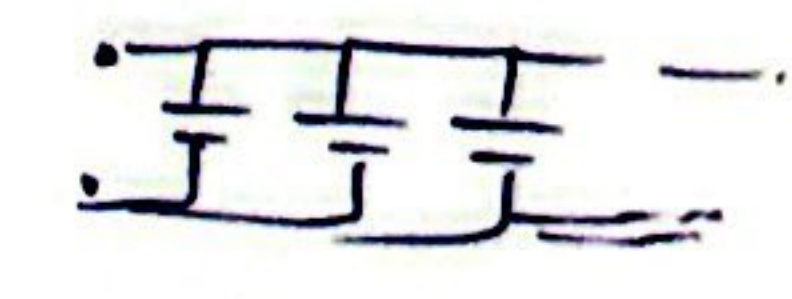

4) Inductor

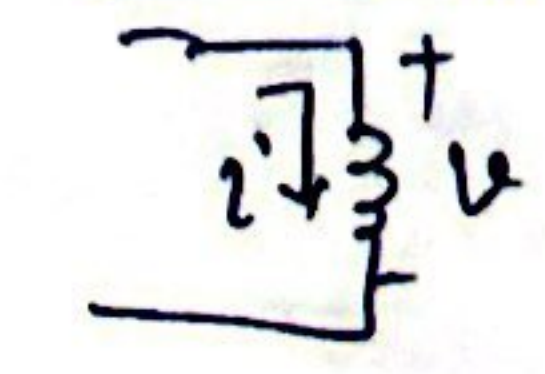

$V = L di/dt$


ability to store energy in moving charges or magnetic field

⇒ Energy stored: $E = \int_{t_0}^t V i dt = \frac{1}{2} L i^2$

⇒ an abrupt change in current requires ∞ Voltage


⇒ series: $L_1 + L_2 + \dots$ Parallel: $\frac{1}{L_{eq}} = \frac{1}{L_1} + \dots$

③ Summary:

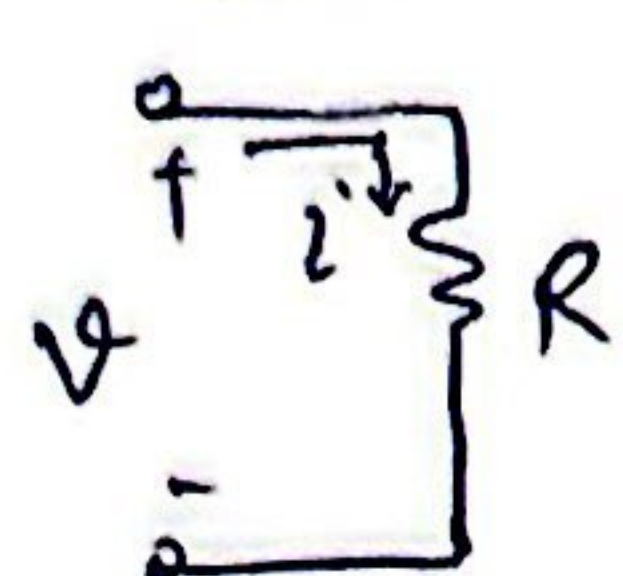


$$V = Ri$$

$$i = V/R$$

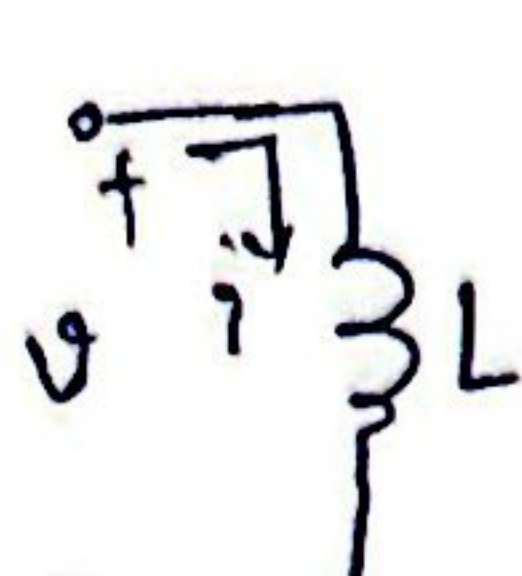

$$V = L \frac{di}{dt}$$
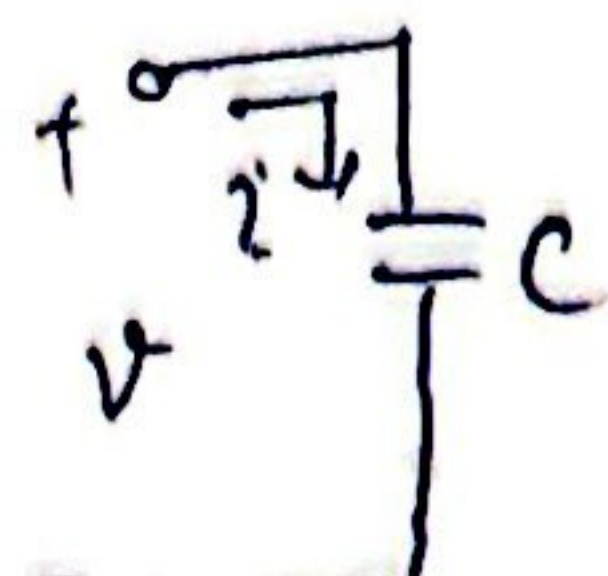
$$i = \frac{1}{L} \int_{-\infty}^t V dt$$





$$i = C \frac{dV}{dt}$$


$$V = \frac{1}{C} \int_{-\infty}^t i dt$$

⇒ Voltage across capacitor & current in an inductor can not change instantaneously.

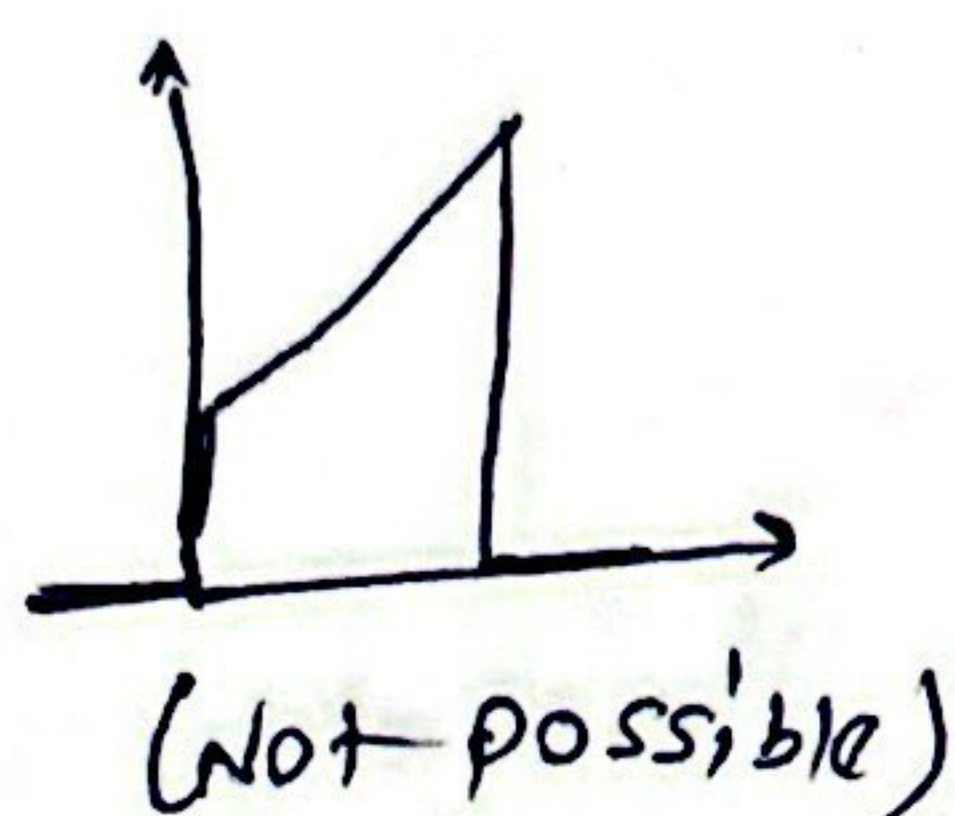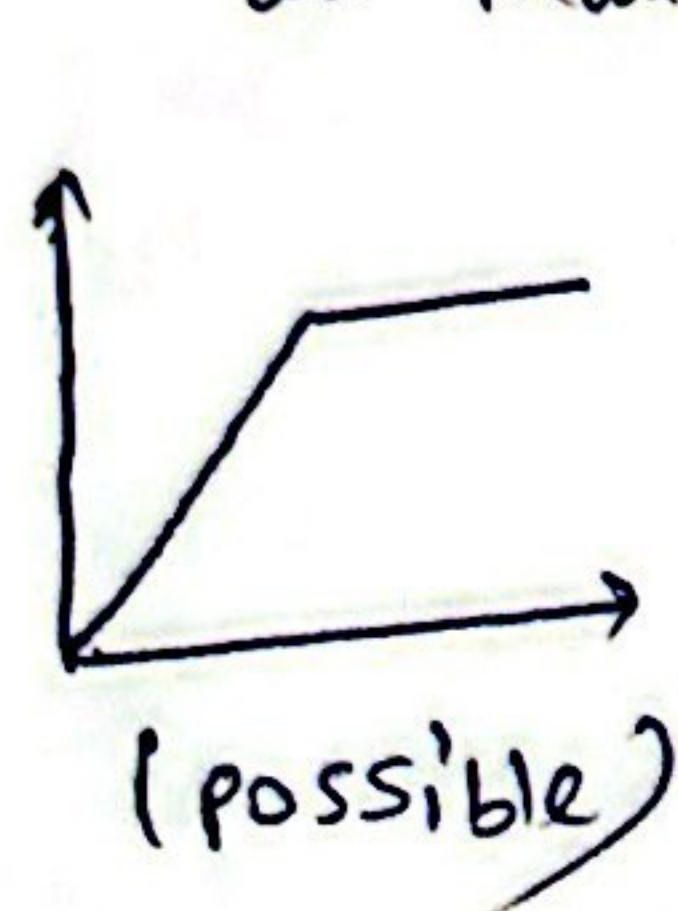Qn: which can be current through an inductor



Qn:

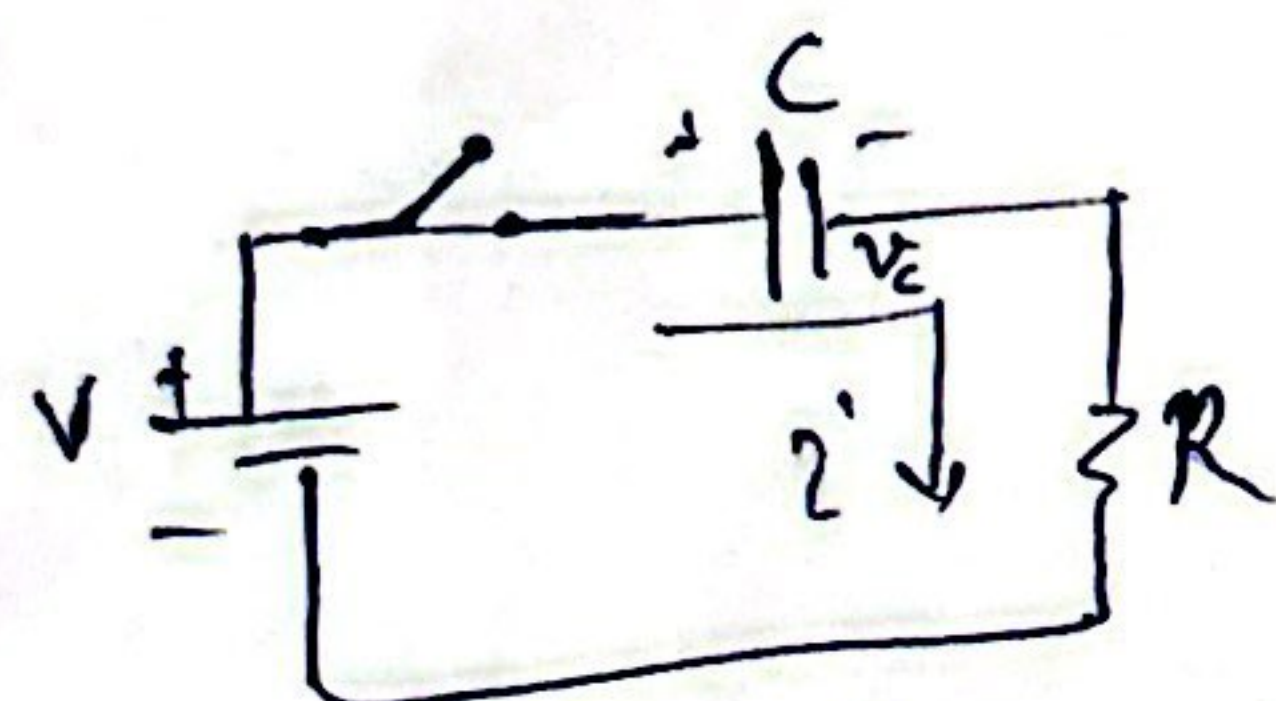


if switch closes at $t = 0$ & cap is initially relaxed, initial condition $i(0^+)$, $V_R(0^+)$, $V_C(0^+)$

$$V_C(0^+) = 0 \Rightarrow i(0^+) = \frac{V}{R}$$

$$\frac{dV_C(0^+)}{dt} = i/C = \frac{V}{RC}$$

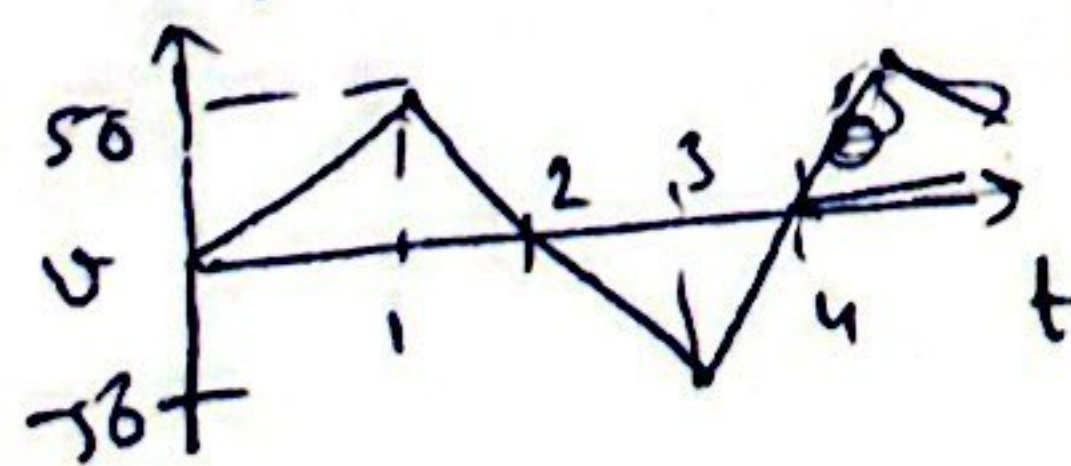Qn: determine the current as fn. of time through a 200 mF whose voltage is



$$V = \begin{cases} 50t & 0 < t < 1 \\ 100 - 50t & 1 < t < 3 \\ -200 + 50t & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

$$i = C \frac{dV}{dt} = \begin{cases} 10 \text{ mA} & 0 < t < 1 \\ -10 \text{ mA} & 1 < t < 3 \\ 10 \text{ mA} & 3 < t < 4 \\ 0 \text{ mA} & \text{otherwise} \end{cases}$$

Linearity: homogeneity & Additivity

1) homogeneity property

$$\text{if } X(t) \rightarrow Y(t)$$

$$\text{then } \alpha X(t) \rightarrow \alpha Y(t)$$

2) Additive property

$$\text{if } X_1(t) \rightarrow Y_1(t) \text{ and}$$

$$X_2(t) \rightarrow Y_2(t)$$


$$\text{then } X_1(t) + X_2(t) \rightarrow Y_1(t) + Y_2(t)$$

Check if R, L, C are linear

KCL - KVL

analyzing circuits


Ex.

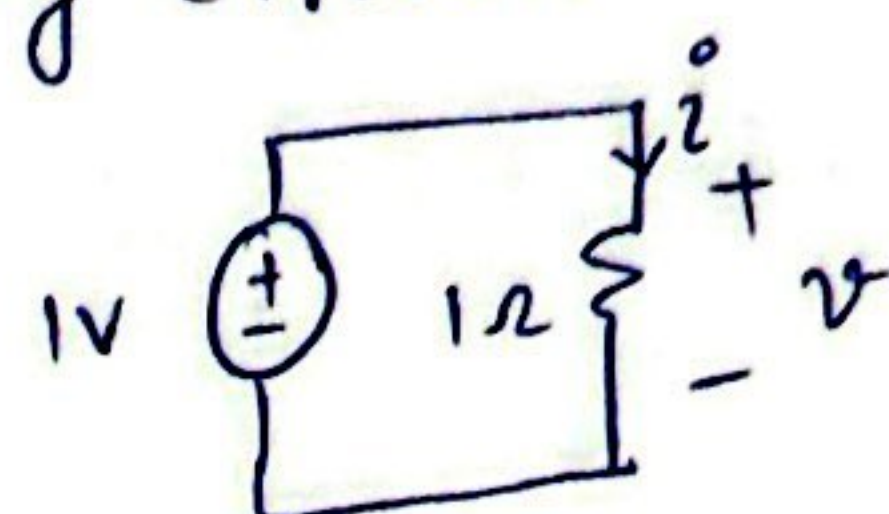

$$V = 1V$$

$$i = \frac{V}{R} = 1A$$


Ex.

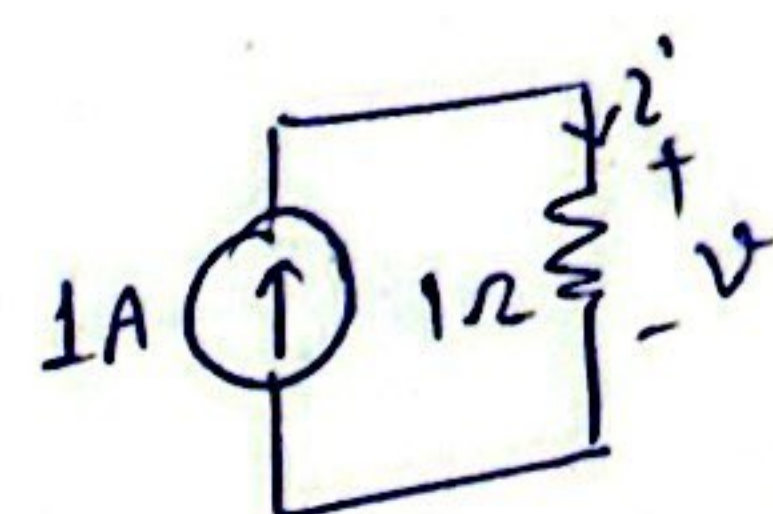

$$i = 1A$$

$$V = i \times R = 1V$$

Qn:

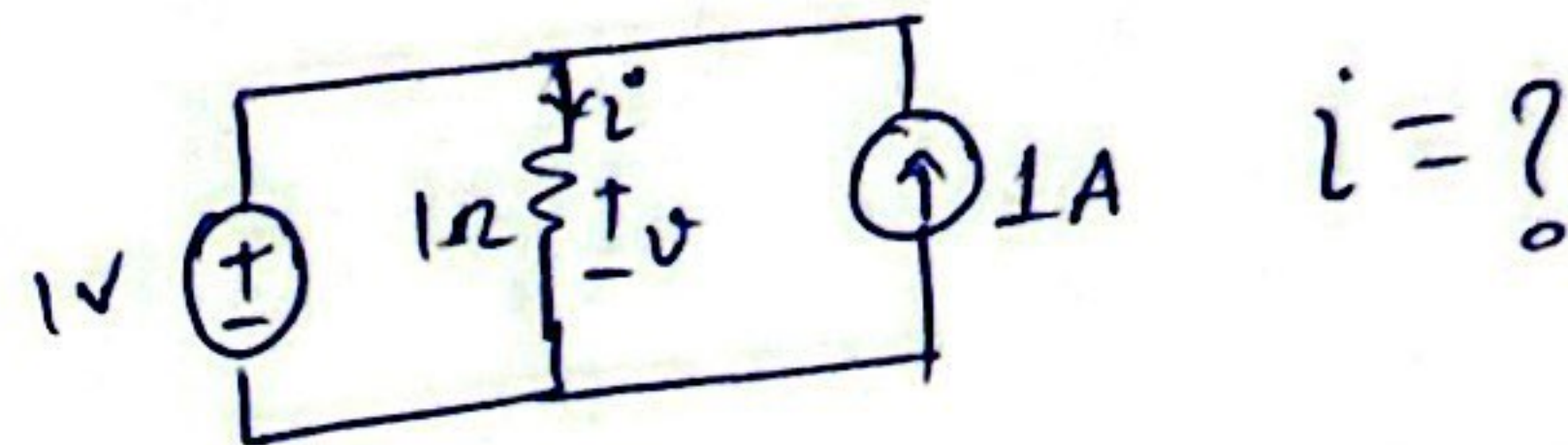

$$i = ?$$


- A) 1A B) 2A C) 0A D) can not determine

⇒ since voltage generated by current source is same as voltage source, voltage source is not providing any current.

⇒ if current source is 2A, then 1A current flows into the voltage source.

More complex ckt's can be analyzed using KVL & KCL

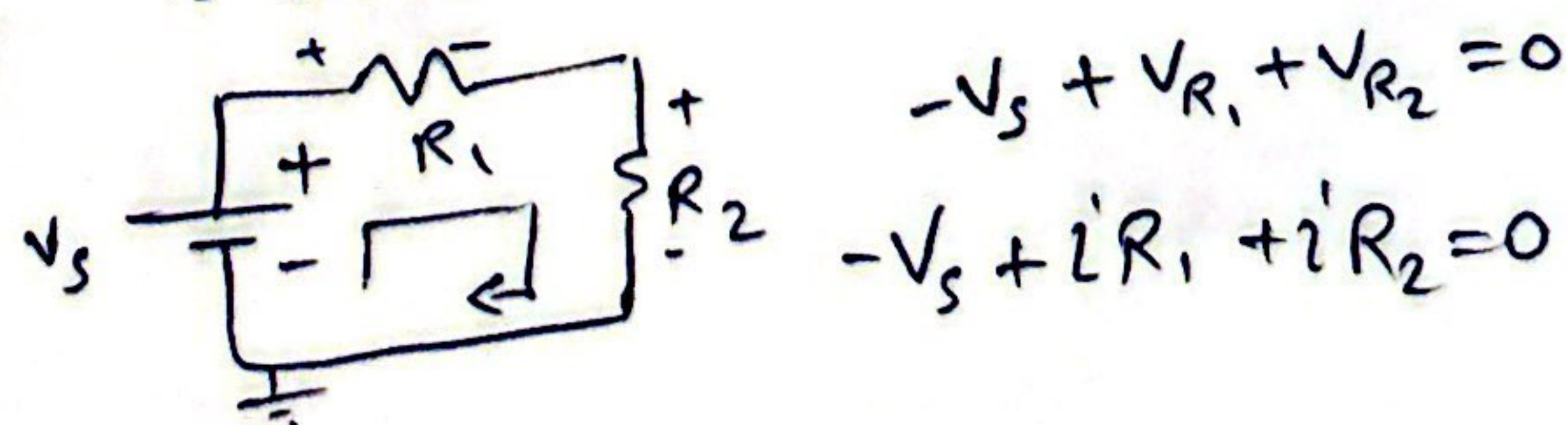KVL: Algebraic sum of all voltages around a closed path is zero



$$-V_s + V_{R1} + V_{R2} = 0$$

$$-V_s + iR_1 + iR_2 = 0$$