
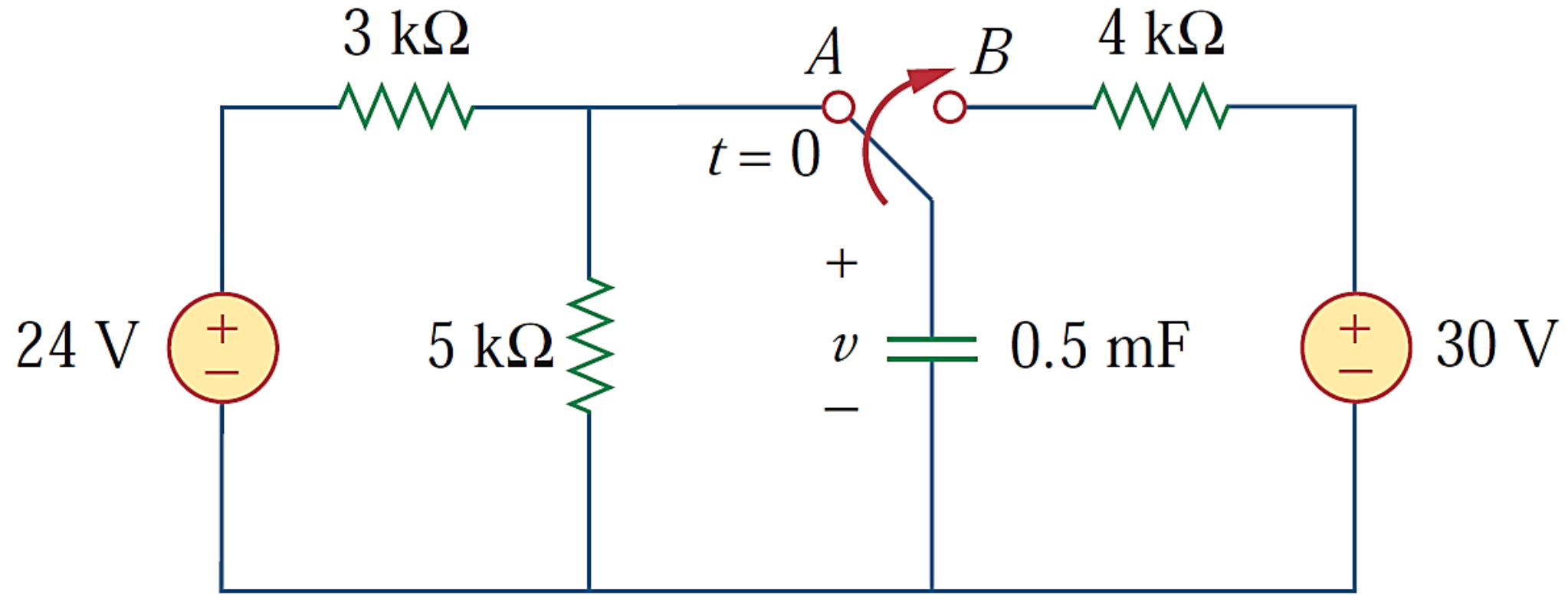


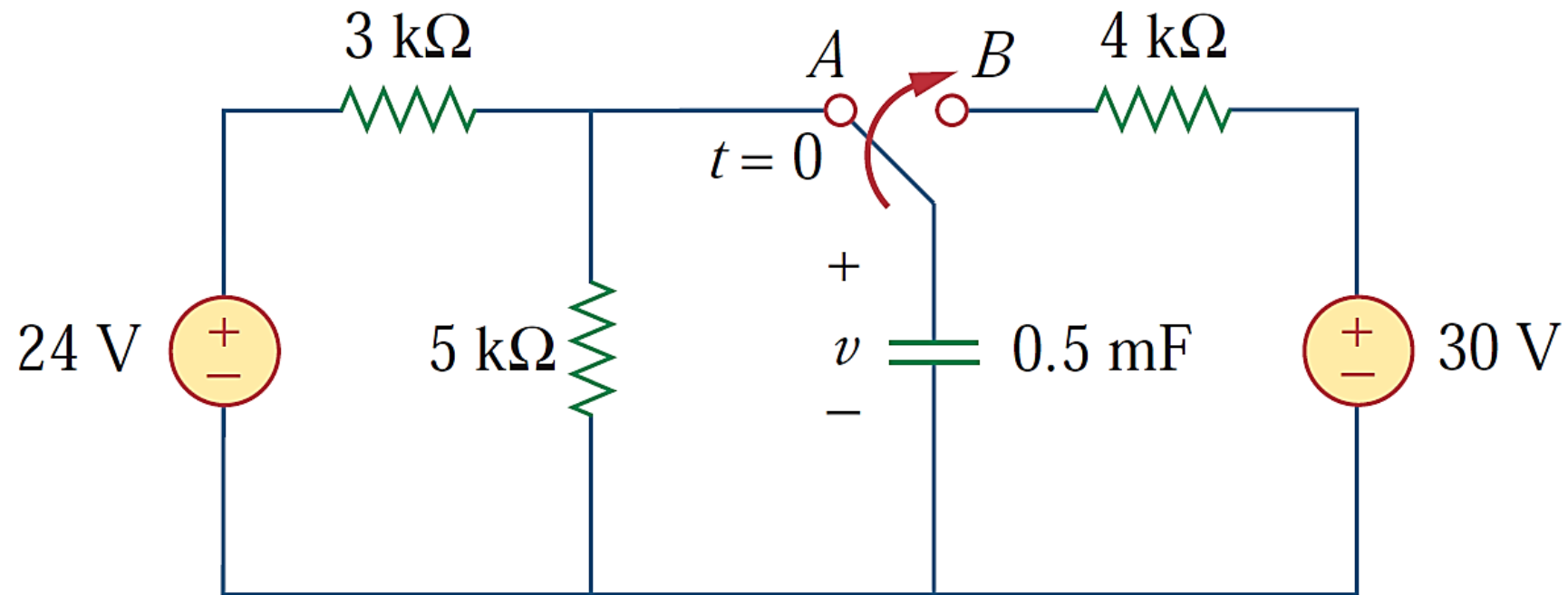Problem 1: The switch in given circuit was in position A for a long time. At $t = 0$, the switch moves to B. Determine the voltage across the capacitor at $t = 1\text{s}$ and 4s .





Solution:

For $t < 0$, the switch is at position A. The capacitor acts like an open circuit to dc, so v is the same as the voltage across the 5kΩ resistor. Hence, the voltage across the capacitor before $t=0$ is obtained by voltage division as,

$$v(0^-) = \frac{5}{5+3}(24) = 15V$$


The capacitor voltage cannot change instantaneously,


$$v(0) = v(0^-) = v(0^+) = 15 \text{ V}$$

For $t > 0$, the switch is in position B. Thevenin resistance connected to the capacitor is $R_{Th} = 4 \text{ k}\Omega$, and the time constant is,

$$\tau = R_{Th}C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

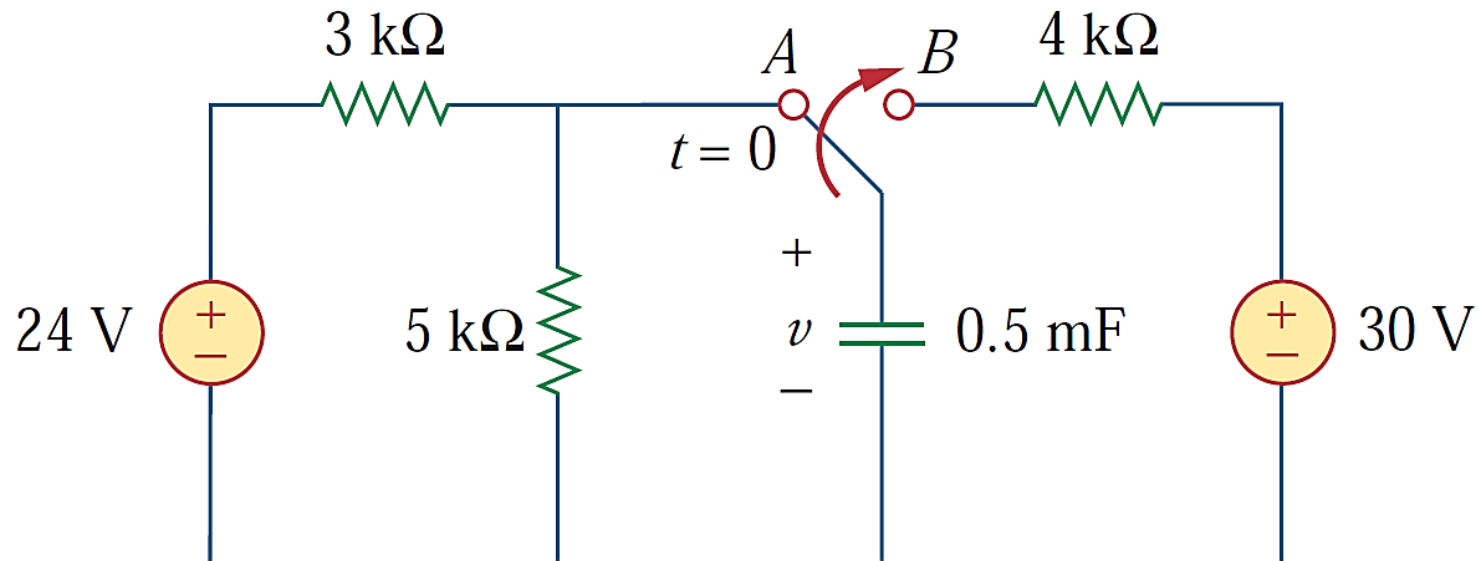$v(\infty) = 30 \text{ V}$ (capacitor acts like an open circuit to dc in steady state)



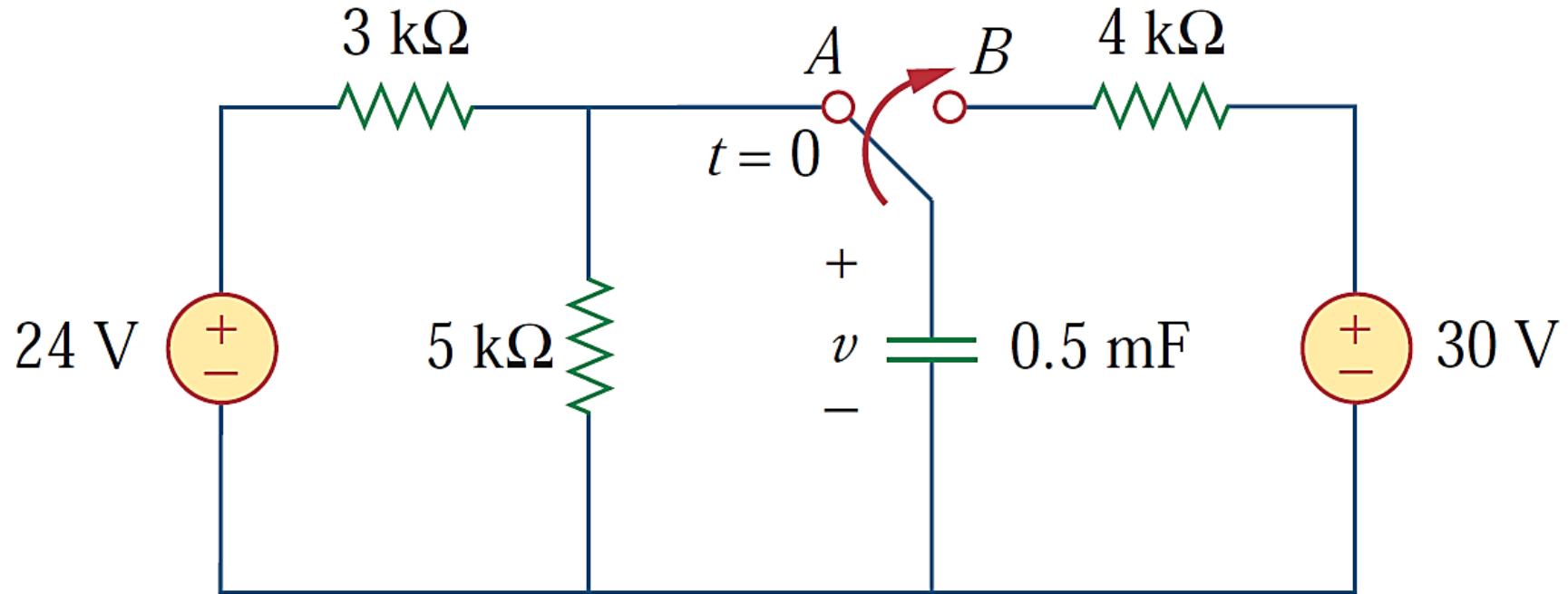



$$\begin{aligned}
 \text{Thus, } v(t) &= v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} \\
 &= 30 + (15 - 30)e^{-t/2} \\
 &= (30 - 15e^{-0.5t}) \text{ V}
 \end{aligned}$$

$$\text{At } t = 1, v(1) = 30 - 15e^{-0.5} = 20.9 \text{ V}$$

$$\text{At } t = 4, v(4) = 30 - 15e^{-2} = 27.97 \text{ V}$$

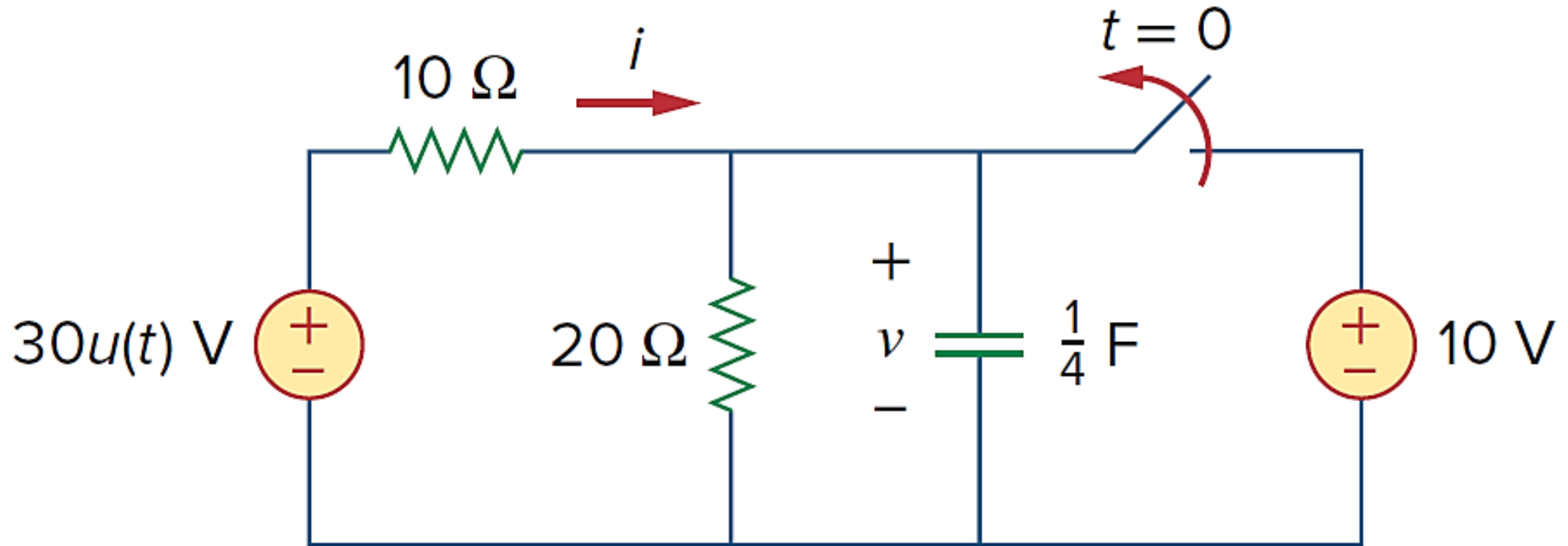Problem 2: In the circuit below, the switch has been closed for a long time and is opened at $t = 0$. Find i and v for all time.



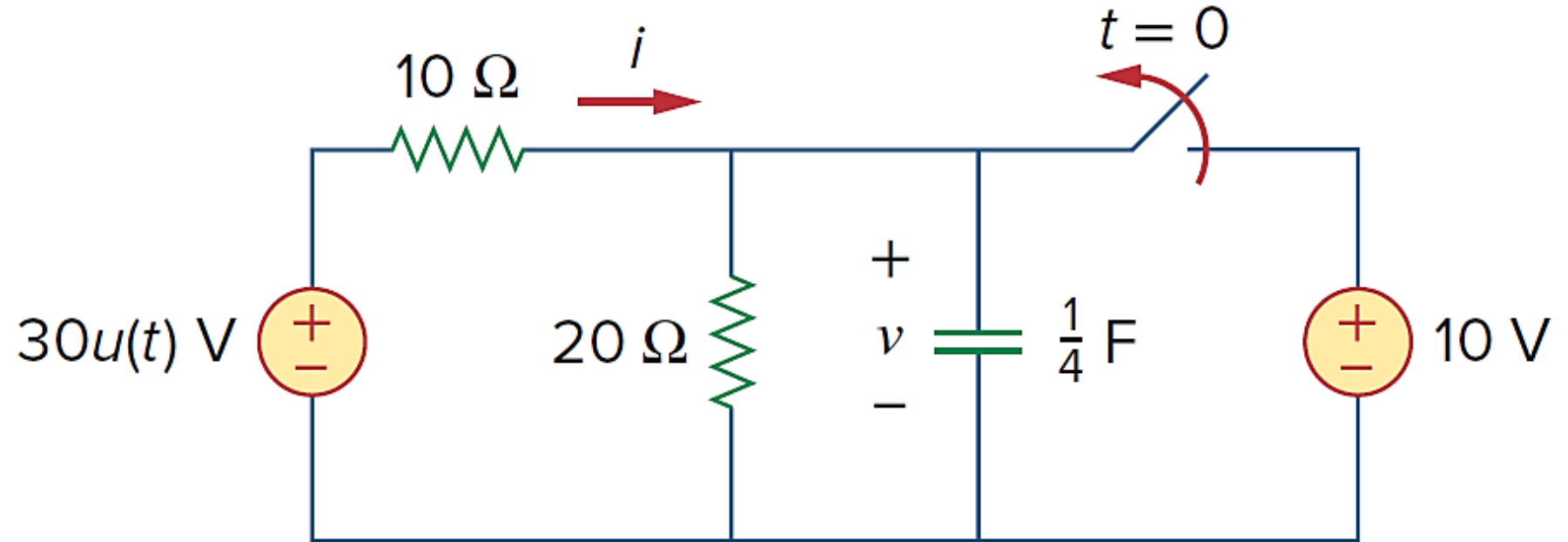


Solution:

Note: The resistor current i can be discontinuous at $t=0$, while the capacitor voltage v has to be continuous.

Hence, it is always better to find v and then obtain i from v .

For $t < 0$:

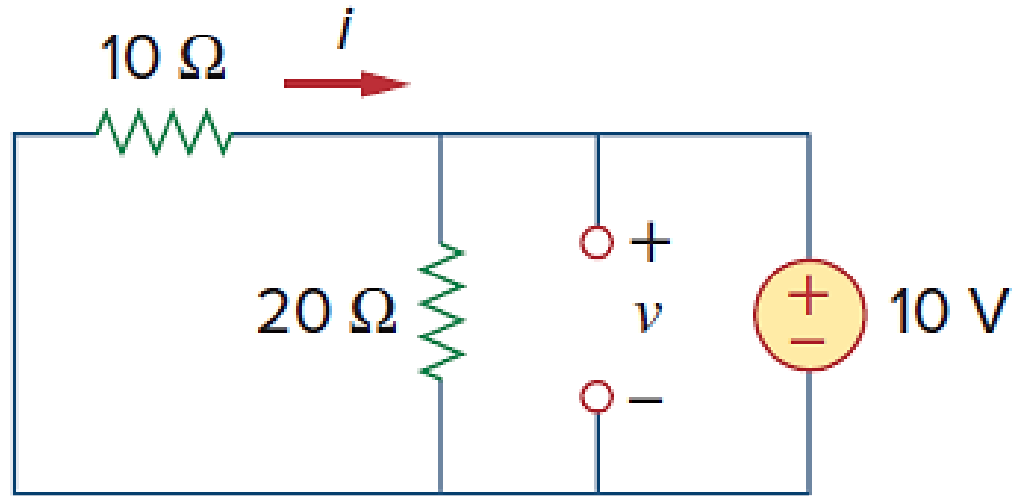

By definition of the unit step function, $30u(t) = \begin{cases} 0 & t < 0 \\ 30 & t > 0 \end{cases}$


For $t < 0$, $v = 10\text{V}$, $i = -\frac{v}{10} = -1\text{A}$

The capacitor voltage cannot change instantaneously, $v(0) = v(0^-) = 10\text{V}$

For $t > 0$, the 10V voltage source is disconnected and the 30V voltage source is now operative

$v(\infty)$ is obtained using voltage division,
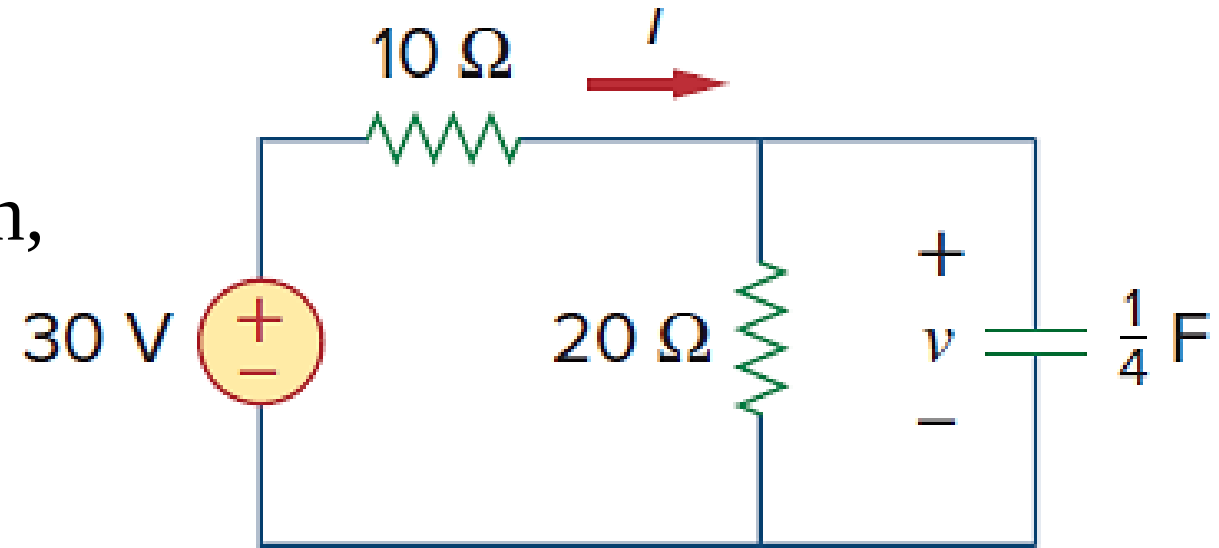
$$v(\infty) = \frac{20}{20+10} (30) = 20V$$



The Thevenin resistance at the capacitor terminals is $R_{Th} = 10 \parallel 20 = 20/3 \Omega$

Time constant is $\tau = R_{Th} C = \frac{20}{3} \cdot \frac{1}{4} = \frac{5}{3} s$


$$\begin{aligned} \text{Thus, } v(t) &= v(\infty) + [v(0) - v(\infty)] e^{-t/\tau} \\ &= 20 + (10 - 20) e^{-(3/5)t} = (20 - 10e^{-0.6t}) V \end{aligned}$$

i is the sum of the currents through the $20\text{-}\Omega$ resistor and the capacitor,

$$i = \frac{v}{20} + C \frac{dv}{dt}$$


$$i = 1 - 0.5e^{-0.6t} + 0.25(-0.6)(-10)e^{-0.6t} = (1 + e^{-0.6t}) \text{ A}$$

Or $v + 10i = 30$ (KVL in outer loop)

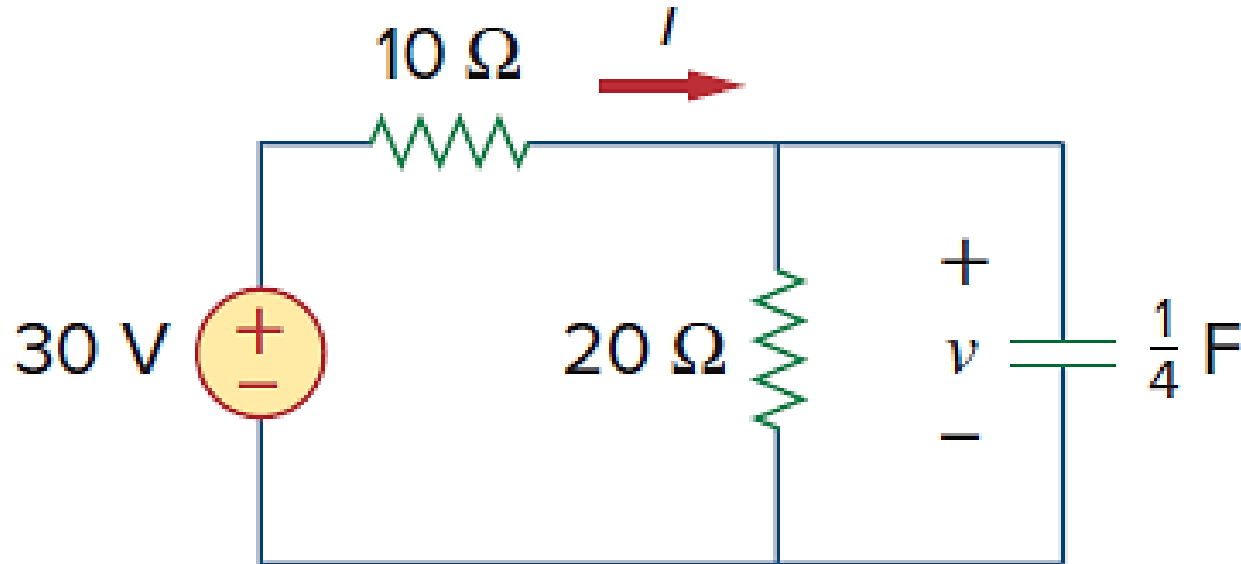

$$v = \begin{cases} 10\text{V} & t < 0 \\ (20 - 10e^{-0.6t})\text{V} & t > 0 \end{cases}$$
$$i = \begin{cases} -1\text{A} & t < 0 \\ (1 + e^{-0.6t})\text{A} & t > 0 \end{cases}$$

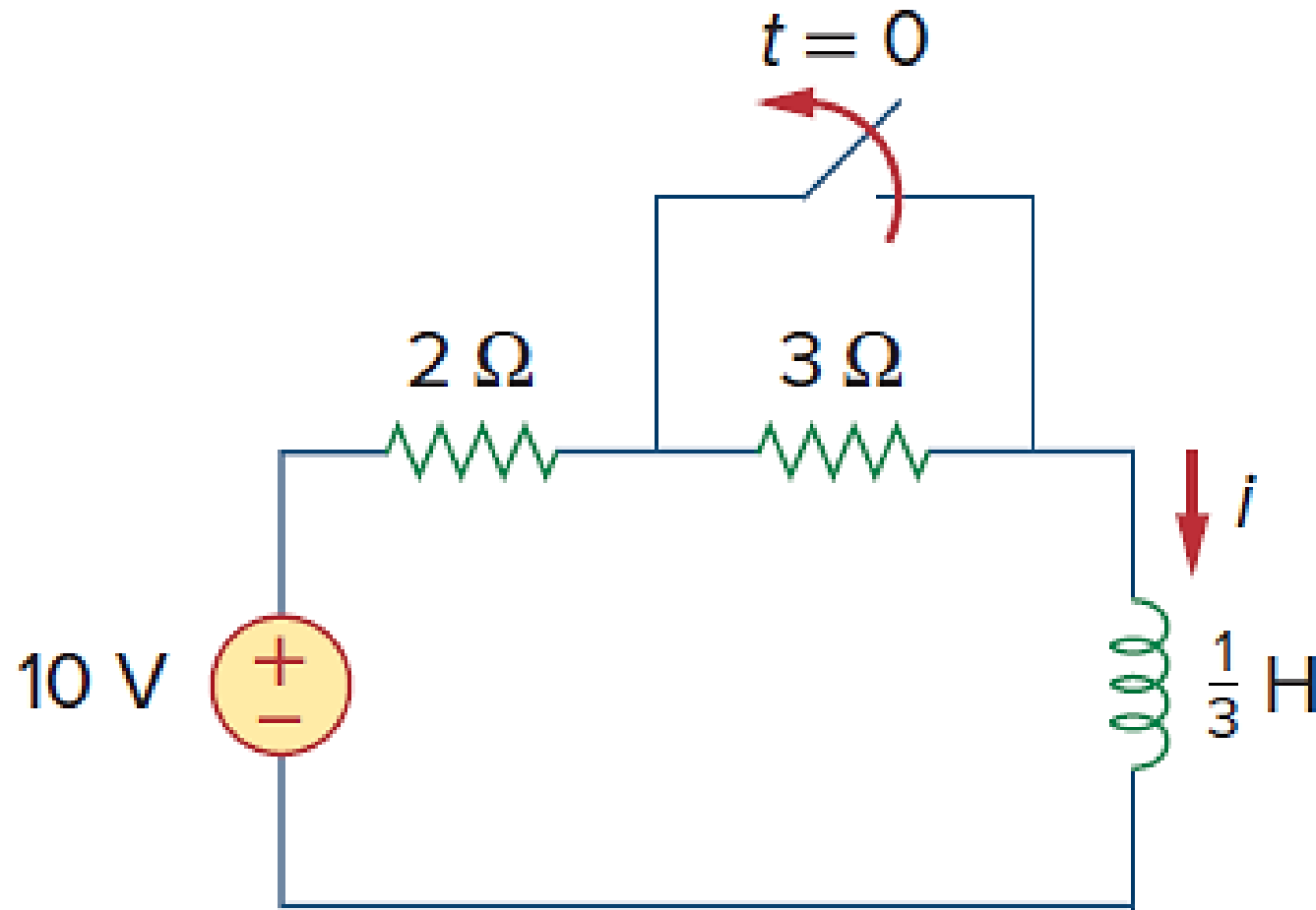Problem 3: Find $i(t)$ in the circuit below for $t > 0$. Assume that the switch has been closed for a long time before opening.




Solution:

For $t < 0$, the $3\text{-}\Omega$ resistor is short-circuited, and the inductor acts like a short circuit. The current through the inductor at $t = 0^-$ is $i(0^-) = 10/2 = 5\text{A}$

Since inductor current cannot change instantaneously $i(0) = i(0^+) = i(0^-) = 5\text{A}$

For $t > 0$, the $3\text{-}\Omega$ resistor comes in series with the $2\text{-}\Omega$ resistor

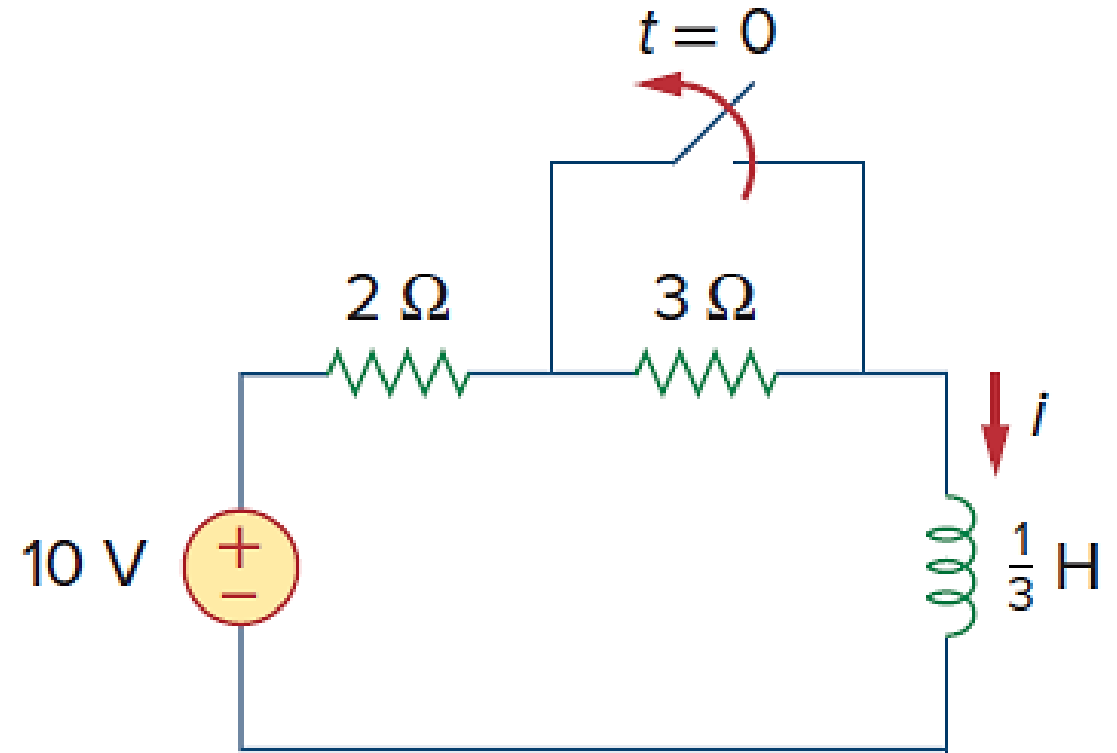The steady-state inductor current is $i(\infty) = \frac{10}{2+3} = 2\text{A}$




The Thevenin resistance across the inductor terminals is

$$R_{TH} = 2 + 3 = 5 \, \Omega$$


Time constant


$$\tau = \frac{L}{R_{TH}} = \frac{\frac{1}{3}}{5} = \frac{1}{15} \, \text{s}$$

$$\begin{aligned} i(t) &= i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \\ &= 2 + (5 - 2)e^{-15t} \\ &= 2 + 3e^{-15t} \, \text{A}, \quad t > 0 \end{aligned}$$

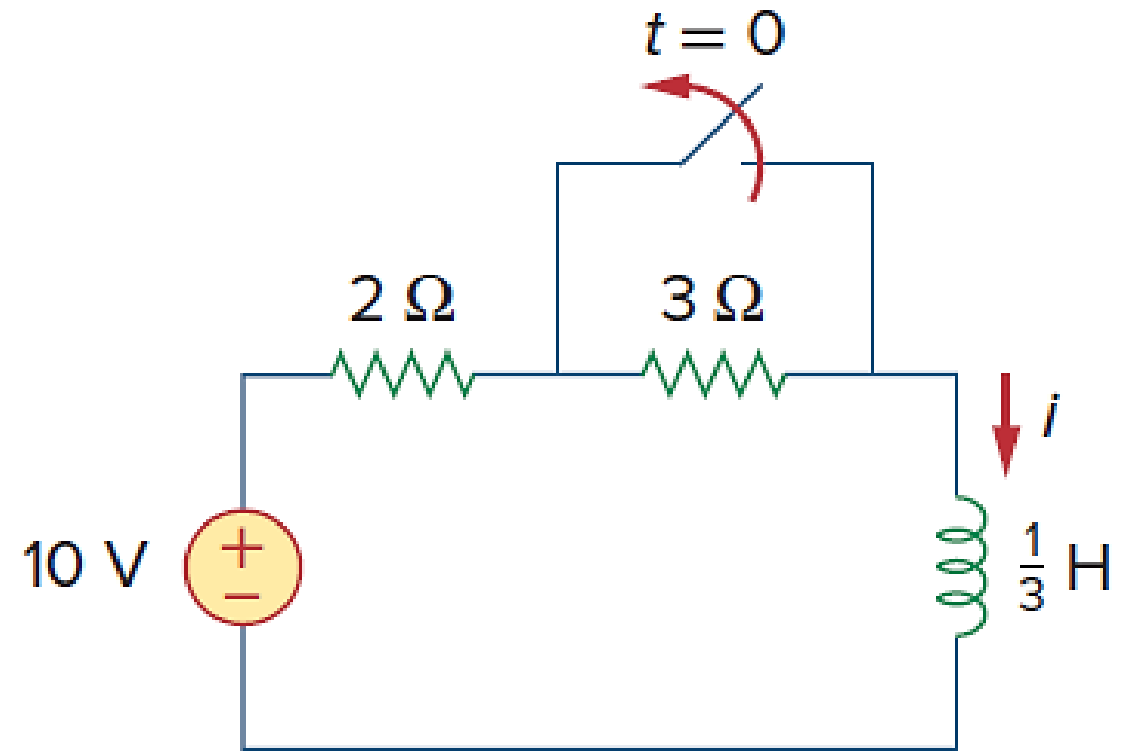

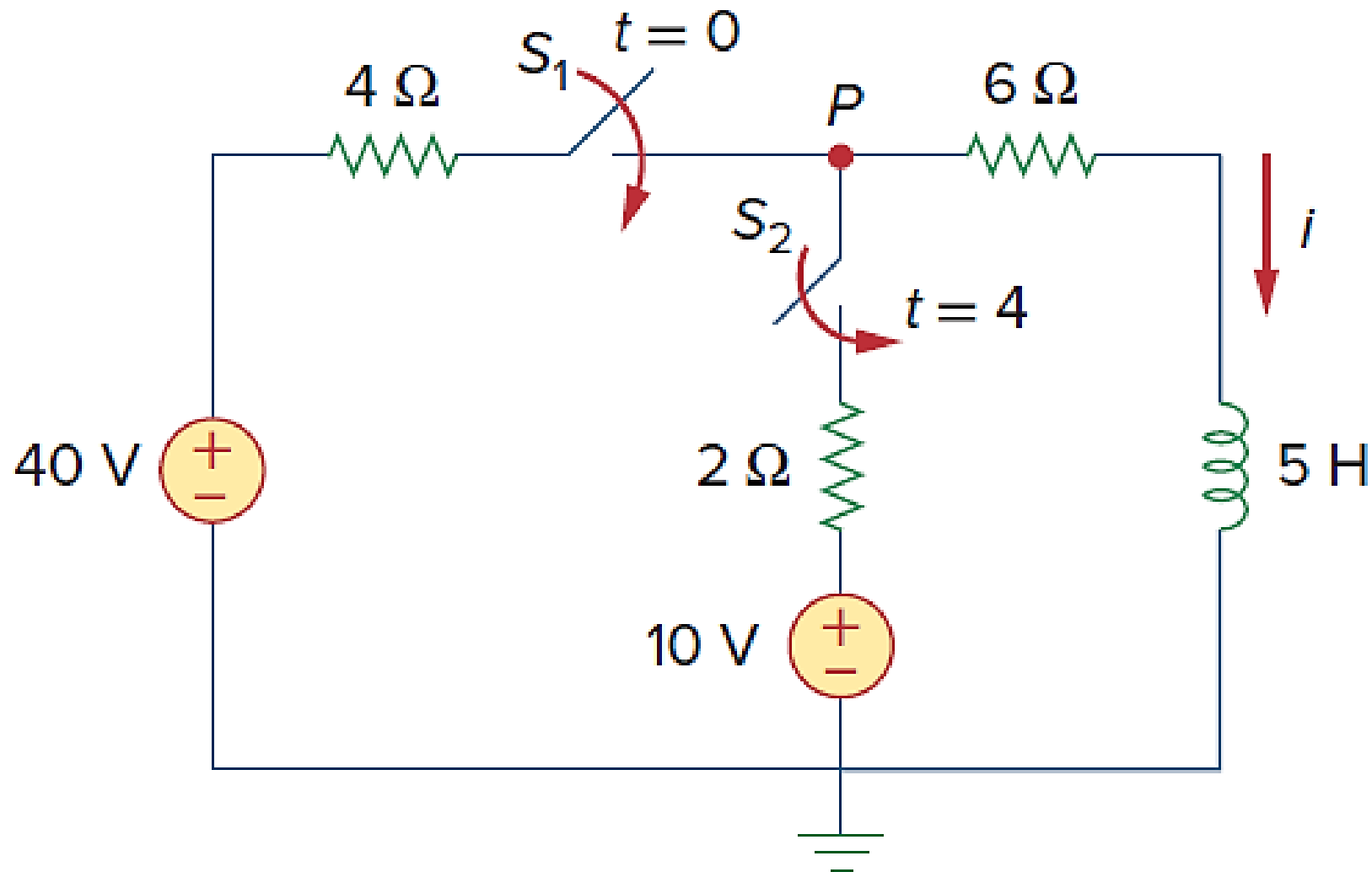Problem 4: At $t = 0$, switch 1 is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i at $t = 2$ s and $t = 5$ s.



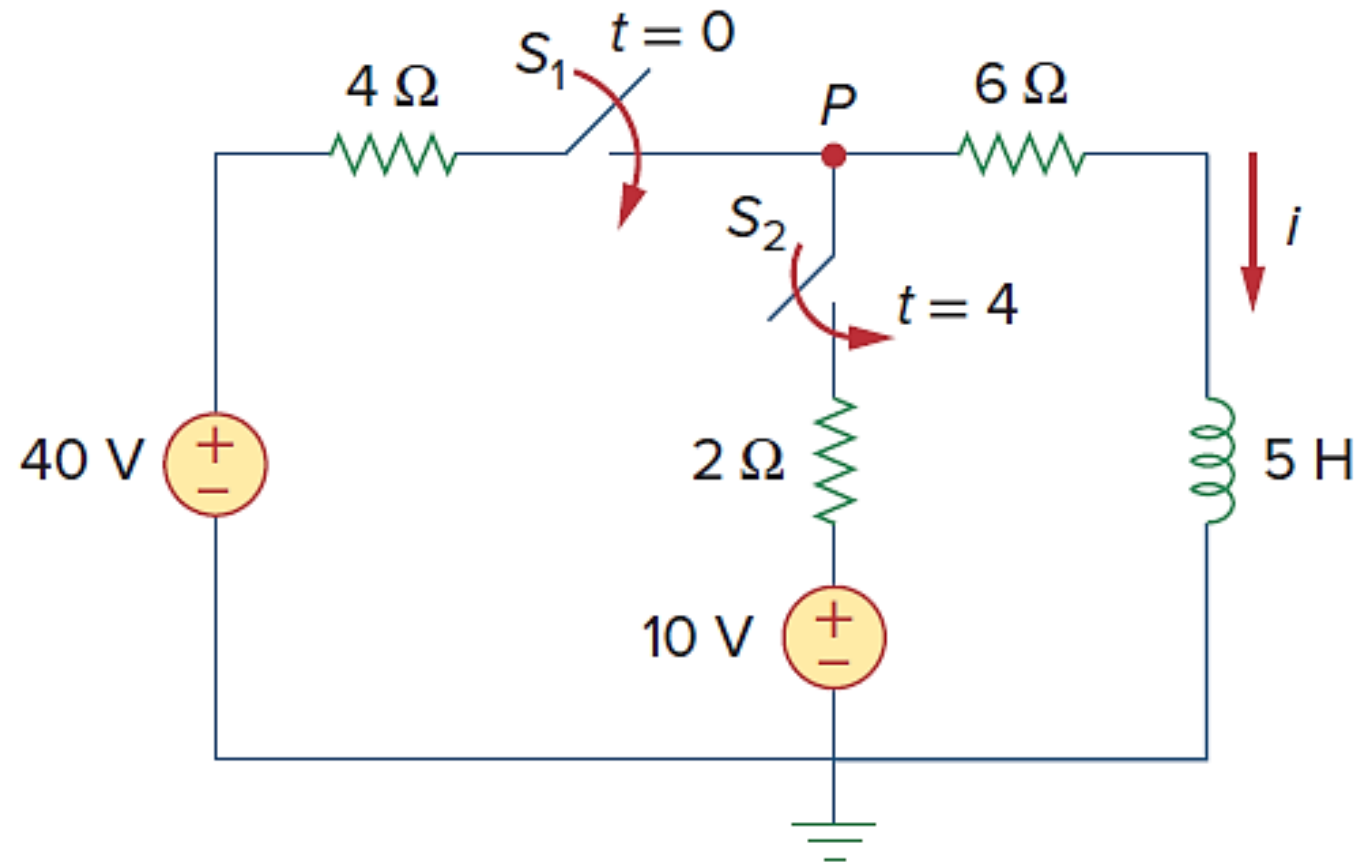

Solution:

Solve for the three time intervals $t \leq 0$, $0 \leq t \leq 4$, and $t \geq 4$ separately. For $t < 0$, switches S_1 and S_2 are open so that $i = 0$. Since the inductor current cannot change instantly, $i(0) = i(0^+) = i(0^-) = 0\text{A}$

For $0 \leq t \leq 4$, S_1 is closed so that the 4- Ω and 6- Ω resistors are in series.


$$i(\infty) = \frac{40}{4+6} = 4\text{A}; R_{Th} = 4+6=10\Omega$$

$$\tau = \frac{L}{R_{TH}} = \frac{5}{10} = \frac{1}{2}\text{s}$$

Thus

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \\ = 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t})\text{ A}$$

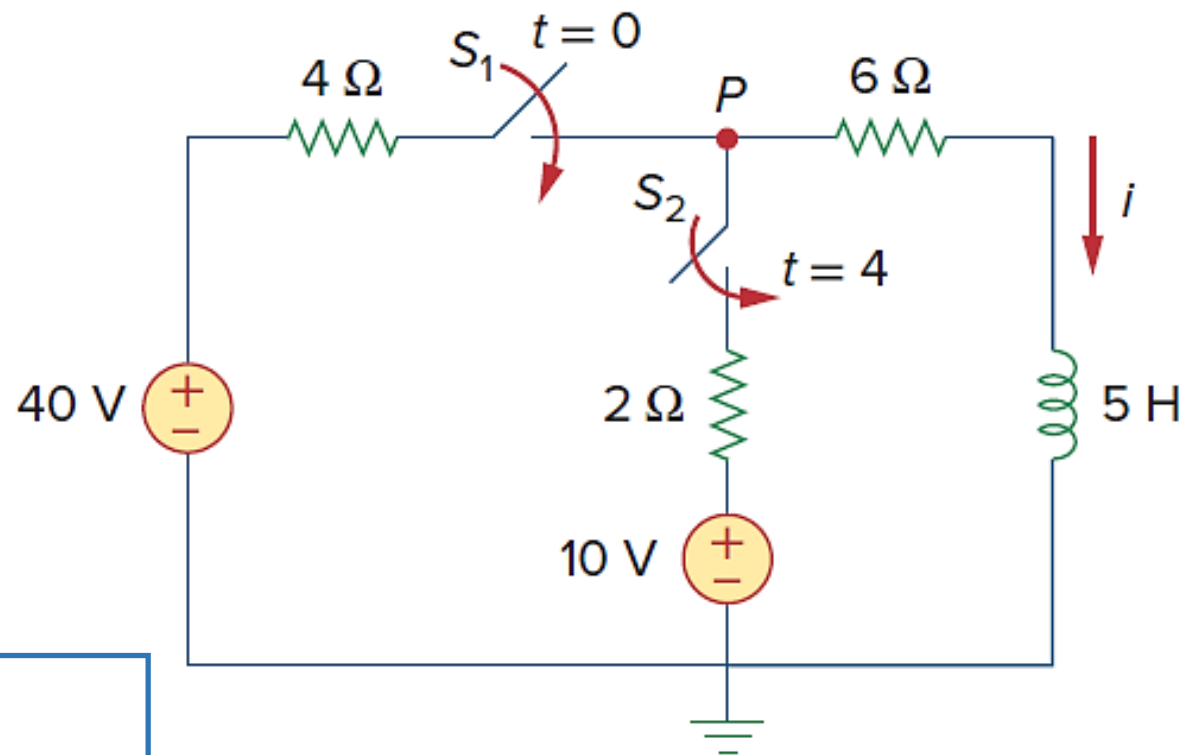For $t \geq 4$, S_1 and S_2 are closed; the 10-V voltage source is also connected into the circuit. The initial current is, $i(4) = 4(1 - e^{-8}) \simeq 4\text{ A}$



To find $i(\infty)$, let v be the voltage at node P ,
Using *KCL*, $\frac{40-v}{4} + \frac{10-v}{2} = \frac{v}{6}$; $v = \frac{180}{11}$ V


$$i(\infty) = \frac{v}{6} = \frac{30}{11} = 2.72 \text{ A}$$

The Thevenin resistance at the inductor terminals is $R_{Th} = 4 \parallel 2 + 6 = (22/3) \Omega$

Time constant

$$\tau = \frac{L}{R_{TH}} = \frac{5}{\frac{22}{3}} = \frac{15}{22} \text{ s}$$
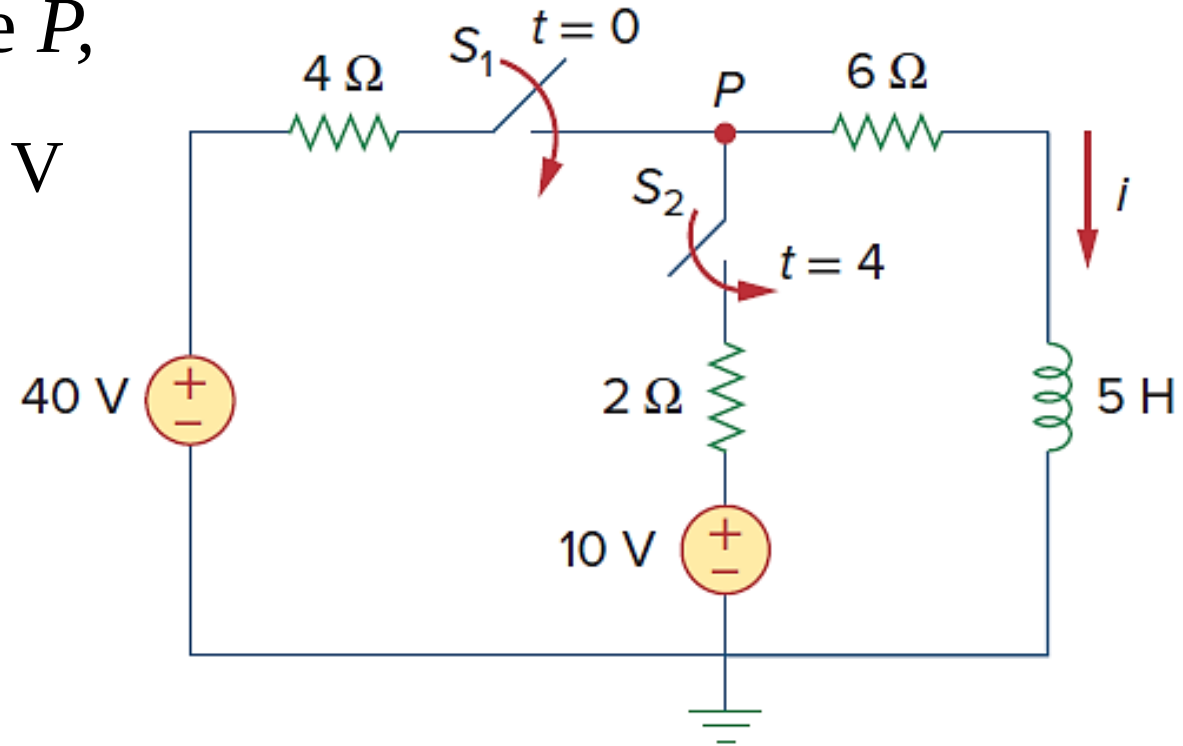
$$\begin{aligned} i(t) &= i(\infty) + [i(4) - i(\infty)]e^{-(t-4)/\tau}, \quad \text{for } t \geq 4 \\ &= 2.727 + (4 - 2.727)e^{-(t-4)/\tau} \quad (\tau = 15/22) \\ &= 2.727 + 1.273e^{-1.4667(t-4)} \end{aligned}$$



Putting everything together,

$$i(t) = \begin{cases} 0 & t \leq 0 \\ 4(1 - e^{-2t}) & 0 \leq t \leq 4 \\ 2.727 + 1.273e^{-1.4667(t-4)} & t \geq 4 \end{cases}$$

At $t = 2\text{s}$, $i(2) = 4(1 - e^{-4}) = \mathbf{3.93\text{ A}}$

At $t = 5\text{s}$, $i(5) = 2.727 + 1.273e^{-1.4667} = \mathbf{3.02\text{ A}}$