

NUMERICAL PROBLEMS

Q1. Calculate the line currents in the three-wire Y-Y system of Fig. 1.

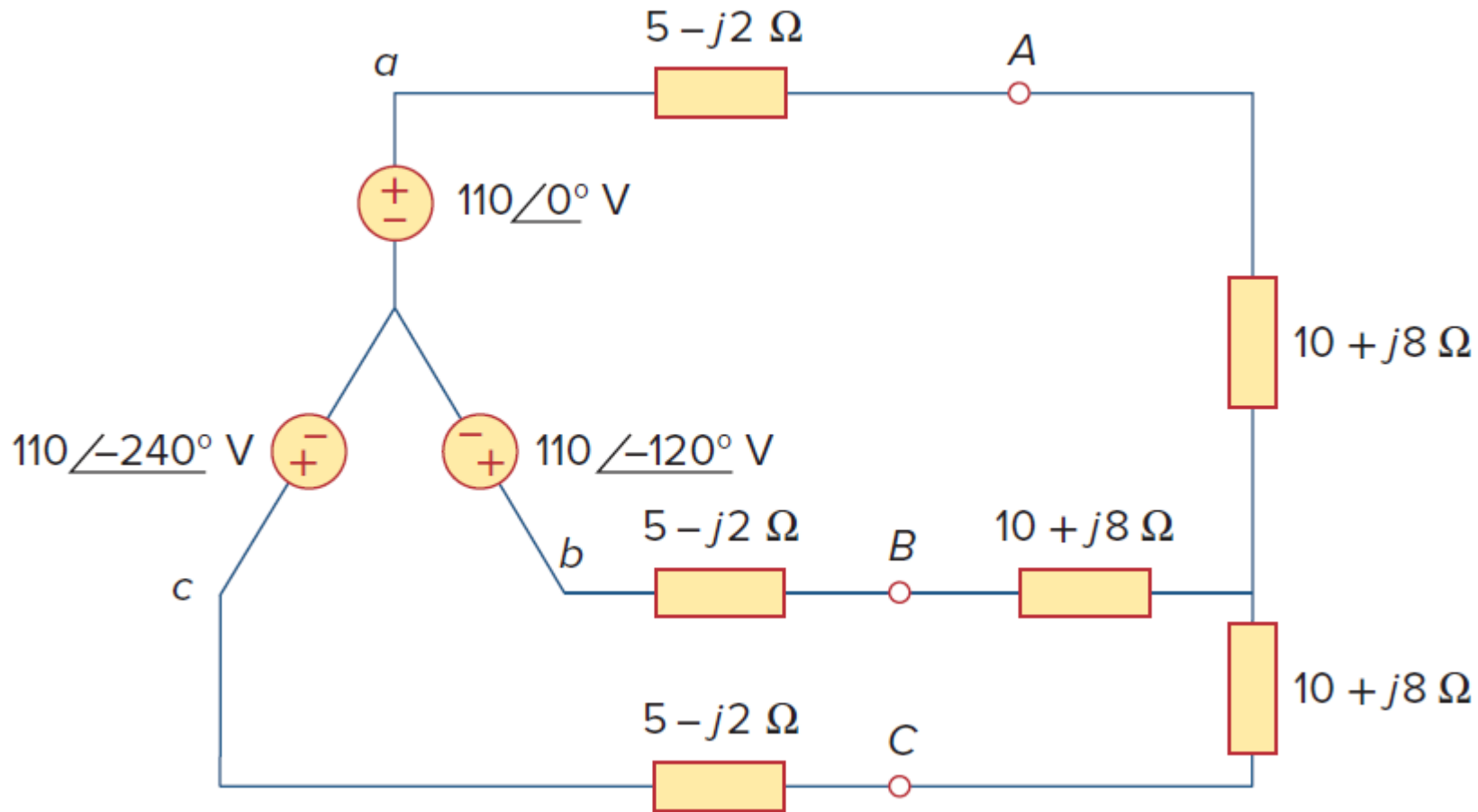


Fig. 1. For Q1.



NUMERICAL PROBLEMS

Ans. The three-phase circuit shown in the figure is balanced; we may replace it with its single-phase equivalent circuit.

We obtain I_a from the single-phase analysis as,

$$I_a = \frac{V_{an}}{Z_Y}$$

where

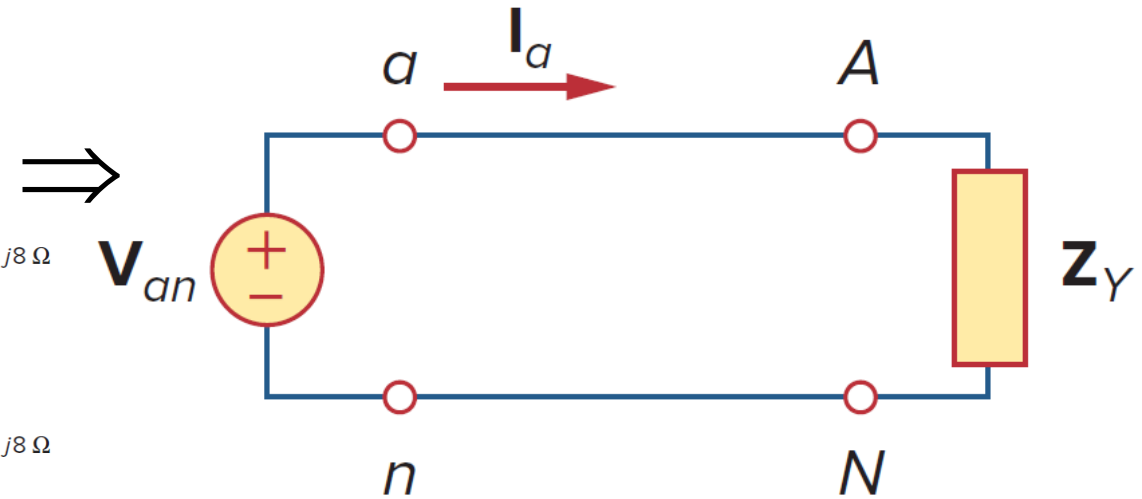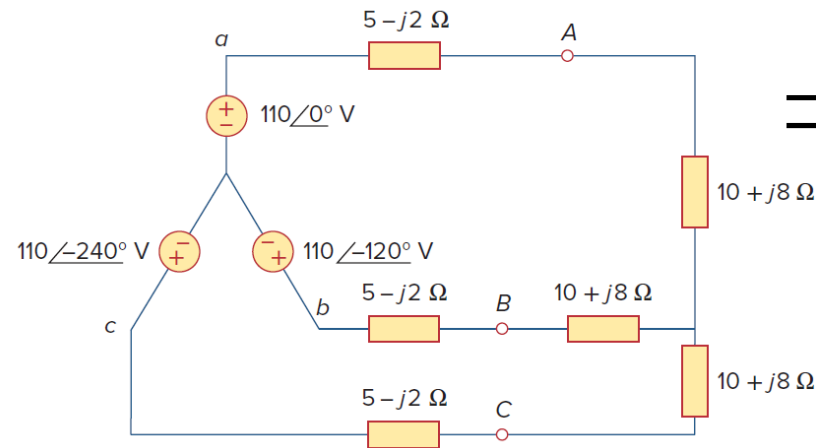

A single-phase equivalent circuit of balanced Y-Y connection

$$\begin{aligned} Z_Y &= (5 - j2) + (10 + j8) = (15 + j6) \\ &= 16.155 \angle 21.8^\circ \end{aligned}$$

NUMERICAL PROBLEMS


Hence,

$$I_a = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$$

In as much as the source voltages in Fig. 1 are in positive sequence, the line currents are also in positive sequence:

$$I_b = I_a \angle -120^\circ = 6.81 \angle -141.8^\circ \text{ A}$$
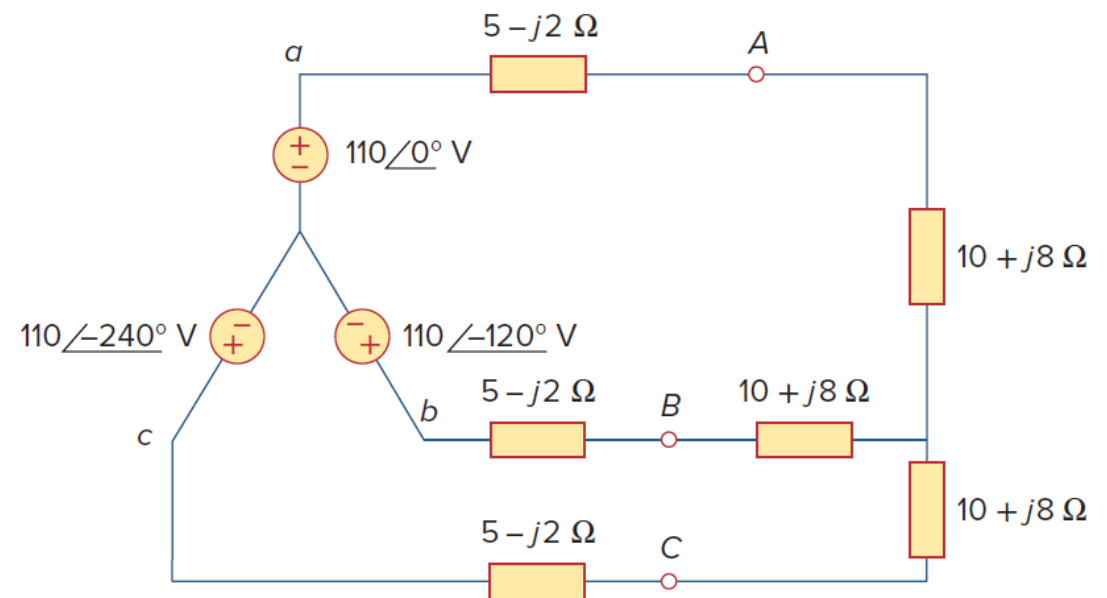
$$I_c = I_a \angle -240^\circ = 6.81 \angle 98.2^\circ \text{ A}$$



NUMERICAL PROBLEMS

Q1. A balanced *abc*-sequence Y-connected source with $V_{an} = 100\angle 10^\circ$ V is connected to a Δ -connected balanced load $(8 + j4) \Omega$ per phase. Calculate the phase and line currents.

Ans.

The load impedance is:

$$Z_{\Delta} = 8 + j4 = 8.944\angle 26.57^\circ \Omega$$

If the phase voltage $V_{an} = 100\angle 10^\circ$ V, then the line voltage is

$$V_{ab} = V_{an} \sqrt{3}\angle 30^\circ = 173.2\angle 40^\circ \text{ V} = V_{AB}$$

NUMERICAL PROBLEMS

The phase currents are,

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{173.2 \angle 40^{\circ}}{8.944 \angle 26.57^{\circ}} = 19.36 \angle 13.43^{\circ} \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^{\circ} = 19.36 \angle -106.57^{\circ} \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^{\circ} = 19.36 \angle 133.43^{\circ} \text{ A}$$

The line currents are,

$$I_a = I_{AB} \sqrt{3} \angle -30^{\circ} = 33.53 \angle -16.57^{\circ} \text{ A}$$

$$I_b = I_a \angle -120^{\circ} = 33.53 \angle -136.57^{\circ} \text{ A}$$

$$I_c = I_a \angle +120^{\circ} = 33.53 \angle 103.43^{\circ} \text{ A}$$

NUMERICAL PROBLEMS

Q1. A balanced Δ -connected load with impedance $20 - j15 \Omega$ is connected to a Δ -connected, positive-sequence generator having $V_{ab} = 330 \angle 0^\circ \text{ V}$. Calculate the phase currents of the load and the line currents.

Ans: The load impedance per phase is $Z_{\Delta} = 20 - j15 = 25 \angle -36.57^\circ \Omega$

Since $V_{AB} = V_{ab}$, the phase currents are,

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{330 \angle 0^\circ}{25 \angle -36.87^\circ} = 13.2 \angle 36.87^\circ \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 13.2 \angle -83.13^\circ \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^\circ = 13.2 \angle 156.87^\circ \text{ A}$$

NUMERICAL PROBLEMS

For a delta load, the line current always lags the corresponding phase current by 30° and has a magnitude $\sqrt{3}$ times that of the phase current. Hence, the line currents are,

$$I_a = I_{AB} \sqrt{3} \angle -30^\circ = 22.86 \angle 6.87^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.13^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 22.86 \angle 126.87^\circ \text{ A}$$

NUMERICAL PROBLEMS

Q1. A balanced Y-connected load with a phase impedance of $40 + j25 \, \Omega$ is supplied by a balanced, positive sequence Δ -connected source with a line voltage of 210 V. Calculate the phase currents. Use V_{ab} as a reference.

Ans:

The load impedance is

$$Z_Y = 40 + j25 = 47.17 \angle 32^\circ \, \Omega$$

and the source voltage is

$$V_{ab} = 210 \angle 0^\circ \, \text{V}$$

When the Δ -connected source is transformed to a Y-connected source,

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ = 121.2 \angle -30^\circ \, \text{V}$$

NUMERICAL PROBLEMS

The line currents are,

$$I_a = \frac{V_{an}}{Z_Y} = \frac{121.2 \angle -30^\circ}{47.12 \angle 32^\circ} = 2.57 \angle -62^\circ \text{ A}$$


$$I_b = I_a \angle -120^\circ = 2.57 \angle -178^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 2.57 \angle 58^\circ \text{ A}$$


which are the same as the phase currents.

Numerical 1

Calculate the line currents.

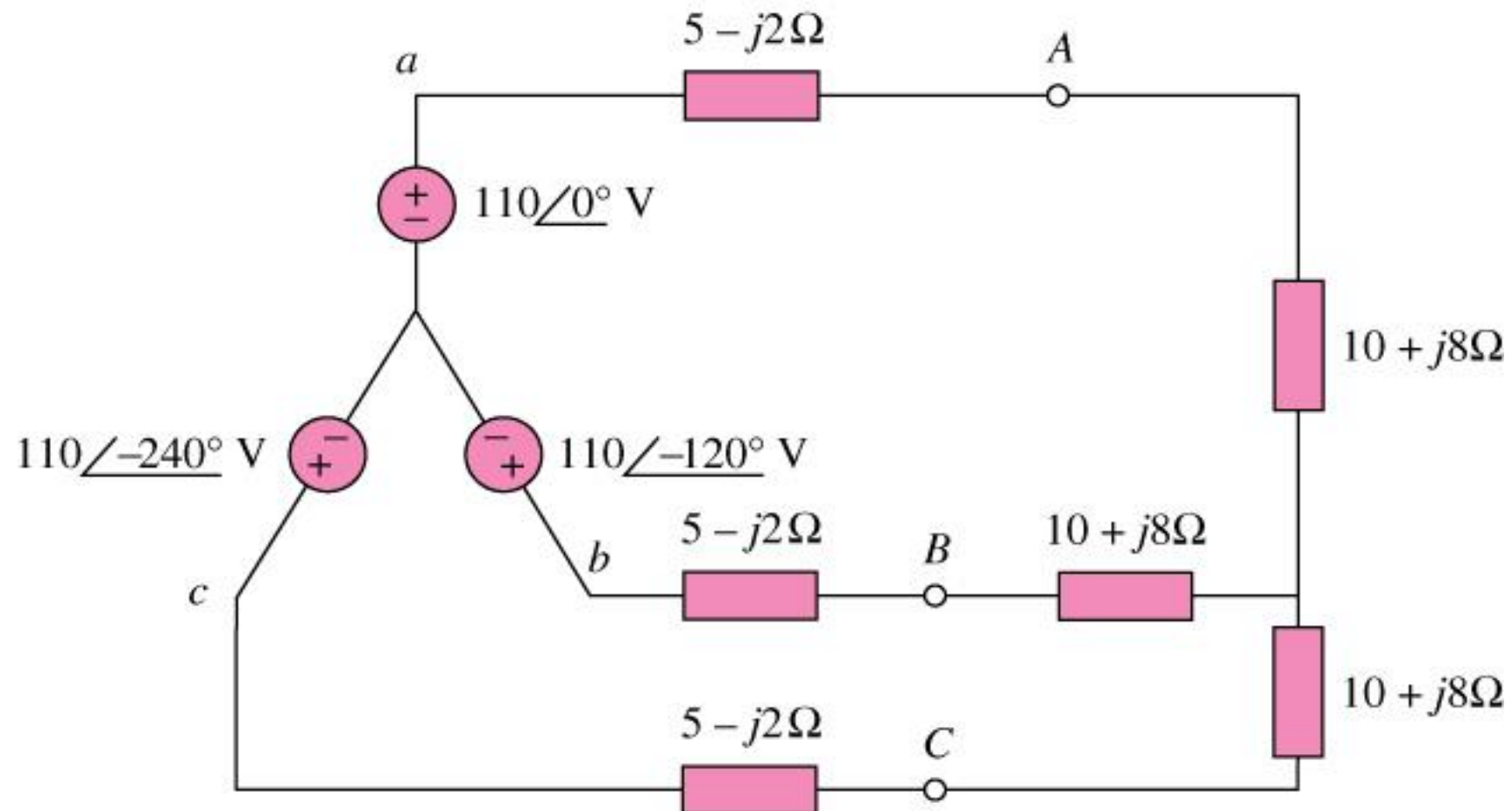

Single Phase Equivalent Circuit

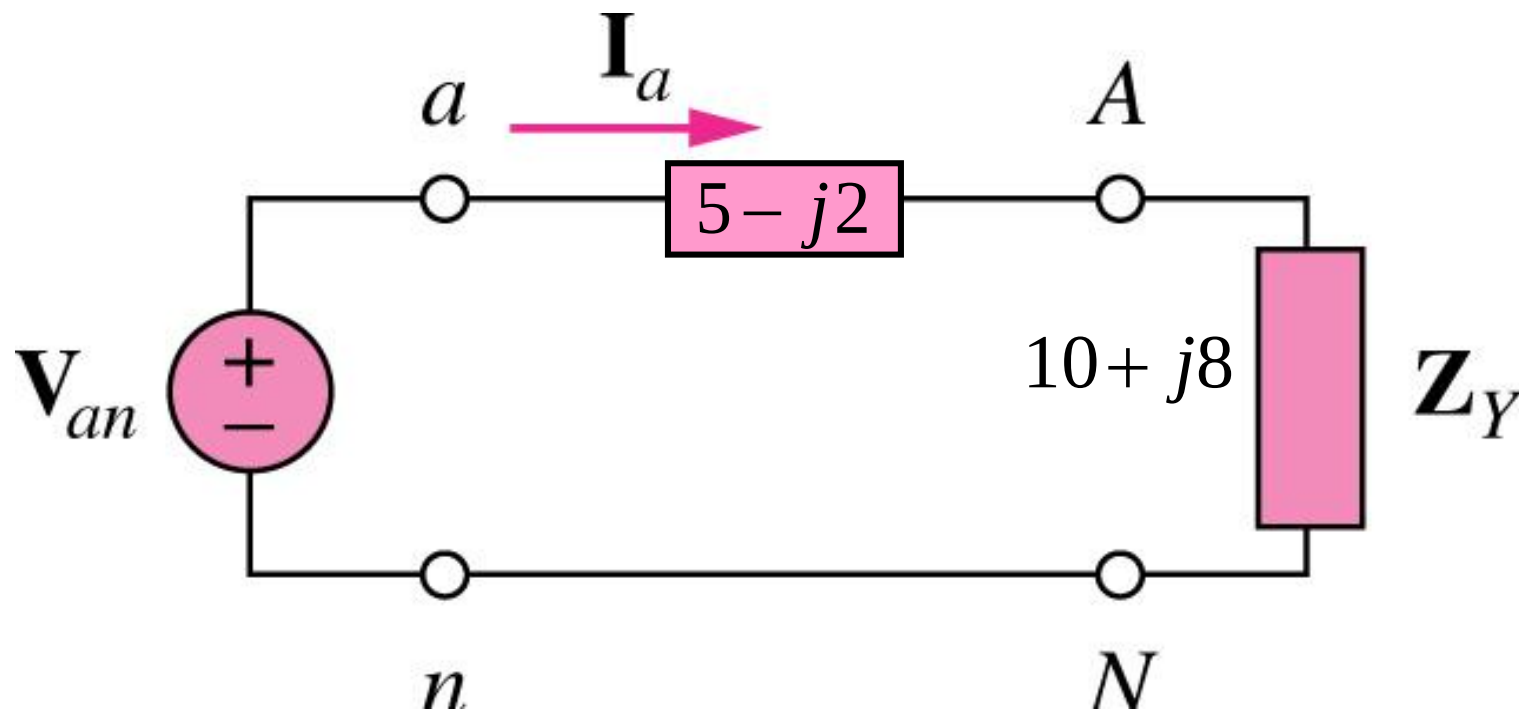

Total impedance per phase $Z_Y = 15 + j6 = 16.155 \angle 21.8^\circ$

$$I_a = \frac{V_{an}}{Z_Y} = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ$$

$$\begin{aligned} I_b &= I_a \angle -120^\circ \\ &= 6.81 \angle -141.8^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} I_c &= I_a \angle -240^\circ \\ &= 6.81 \angle -261.8^\circ = 6.81 \angle 98.2^\circ \text{ A} \end{aligned}$$

Numerical 2

A balanced delta-connected load having an impedance $20-j15\ \Omega$ is connected to a delta-connected, positive-sequence generator having $V_{ab} = 330\angle 0^\circ\text{ V}$.

Calculate the phase currents of the load and the line currents.

Numerical 2

Solution: $Z_{\Delta} = 20 - j15 \, \Omega = 25 \angle -36.87^{\circ}$

$$V_{ab} = 330 \angle 0^{\circ}$$

Phase Currents: $I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{330 \angle 0^{\circ}}{25 \angle -36.87^{\circ}} = 13.2 \angle 36.87^{\circ} \text{ A}$

$$I_{BC} = I_{AB} \angle -120^{\circ} = 13.2 \angle -83.13^{\circ} \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^{\circ} = 13.2 \angle 156.87^{\circ} \text{ A}$$

Line Currents:

$$\begin{aligned} I_a &= I_{AB} \sqrt{3} \angle -30^\circ \\ &= (13.2 \angle 36.87^\circ) (\sqrt{3} \angle -30^\circ) \text{ A} \\ &= 22.86 \angle 6.87^\circ \end{aligned}$$

$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.13^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 22.86 \angle 126.87^\circ \text{ A}$$

Numerical 3

A balanced positive sequence Y-connected source with $V_{an} = 100\angle 10^\circ$ V is connected to a Δ -connected balanced load with impedance $(8 + j4) \Omega$ per phase.

Calculate the phase and line currents at the load.

Numerical 3

Solution: Balanced Y-source with $V_{an} = 100\angle 10^\circ \text{ V}$
Balanced Δ -load with $Z_{\Delta} = 8 + j4 \ \Omega$

$$\text{Phase Current } I_{AB} = \frac{V_{AB}}{Z_{\Delta}}$$

$$\text{Line Voltage } V_{AB} = \sqrt{3} V_{an} \angle 30^\circ$$

$$V_{AB} = 173.2 \angle 40^\circ \text{ V}$$

$$\Rightarrow I_{AB} = \frac{173.2 \angle 40^\circ}{8 + j4} = 19.36 \angle 13.43^\circ$$

Phase Currents:

$$I_{AB} = 19.36 \angle 13.43^\circ \quad A$$

$$I_{BC} = I_{AB} \angle -120^\circ = 19.36 \angle -106.57^\circ \quad A$$

$$I_{CA} = I_{AB} \angle +120^\circ = 19.36 \angle 133.43^\circ \quad A$$

Line Currents:

$$I_a = \sqrt{3} I_{AB} \angle -30^\circ = \sqrt{3} (19.36) \angle (13.43^\circ - 30^\circ)$$

$$I_a = 33.53 \angle -16.57^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 33.53 \angle -136.57^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 33.53 \angle 103.43^\circ \text{ A}$$