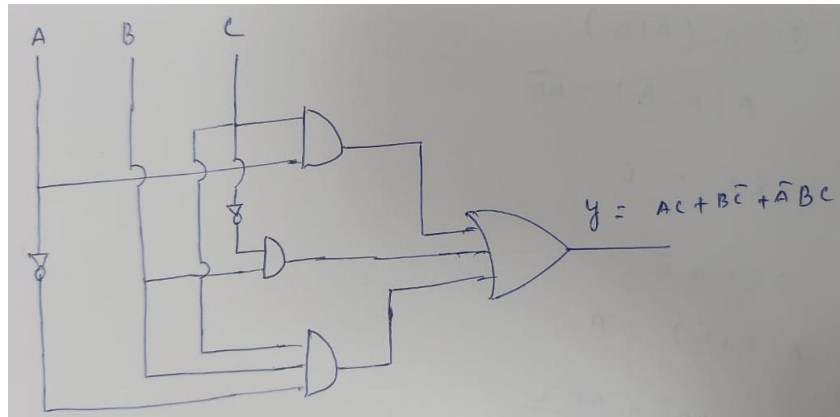



Tutorial 11 Answer Key

1.




2. $B + AC$

3.

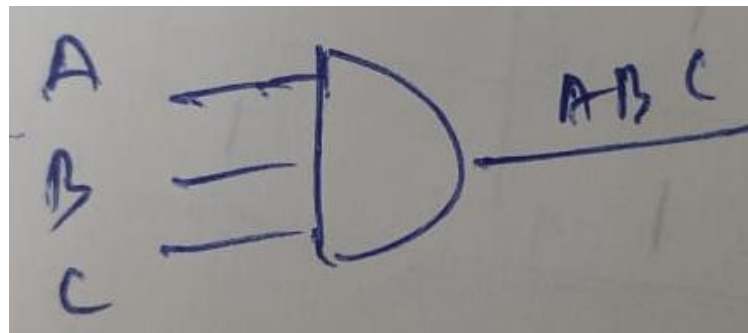


4. (a) 0
 (b) A
 (c) $A(B+C)$
 (d) $A(B+C+D)$


5.

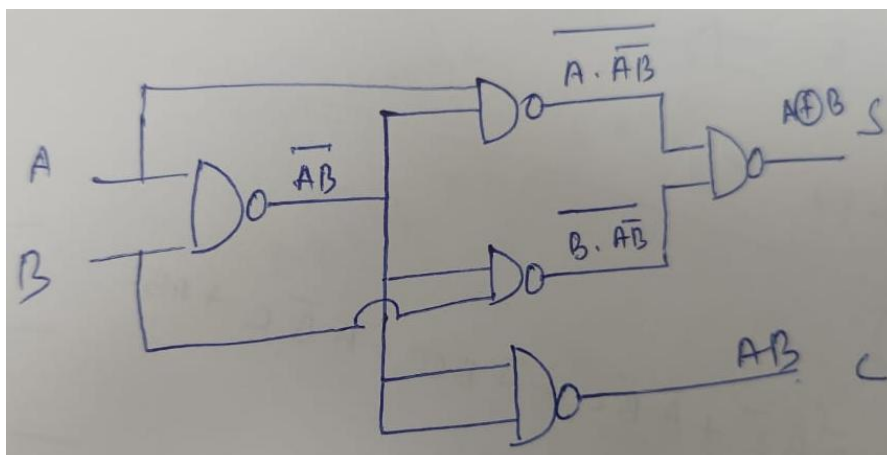

6. (a) $A \oplus B$

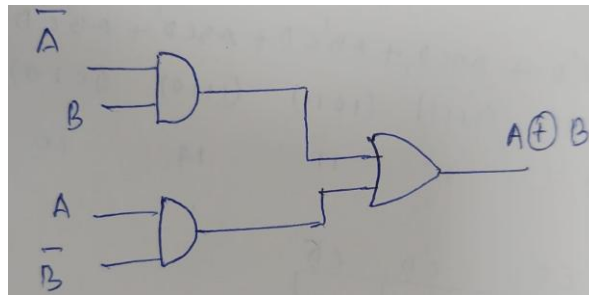

(b)

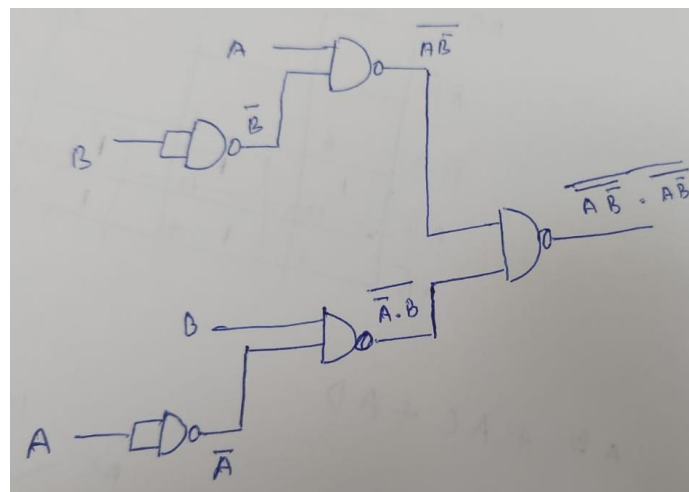


7. (a)

A (input)	B (input)	C (input)	Y (output)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b) $Y = A'B'C' + A'B'C + A'BC + AB'C + ABC' + ABC$

(c) $Y = C + AB + A'B'$

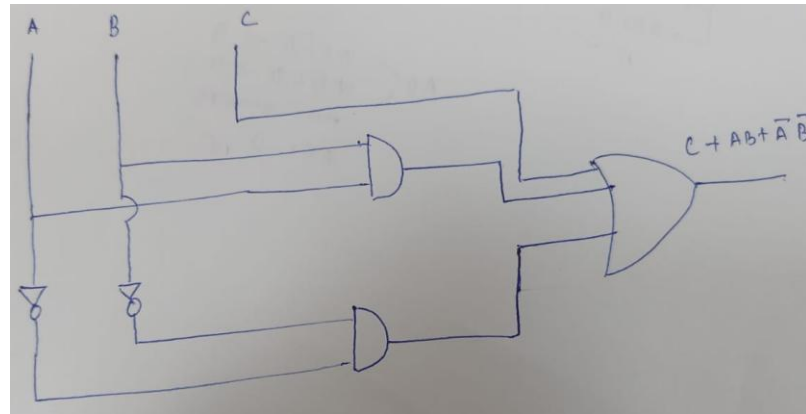

8. $B'D' + BD + AB' + CD$

9. $w'x' + yz$

10. $x'y + xy'$ or $(x \oplus y)$