

Tutorial 9 Answer Key

1. $V_0 = -\frac{R}{L} \int V_1 dt$, Integration function is being performed.
2. (a) $V_x = V_y = V_b \frac{R_2}{R_1 + R_2}$ and $V_0 = \frac{R_2}{R_1} (V_b - V_a)$

(b) Voltage subtraction
(c) $V_0 = 3 + 2\sin\omega t$
3. Slew will not occur.
4. $V_0 = -6 V$
5. $V_0 = 3.1 V$ (*peak to peak*)
6. $2.5 V/\mu s$
7. (a) $V_0 = 8 V$ $I_0 = 1.47 mA$

(b) $\frac{8}{3} < v_a < \frac{32}{3}$ (*volts*)
8. $V_0 = -8 V$, $I_0 = -2 mA$
9. $V_0 = 8 V$
10. $V_0 = -(83.3 \sin 2t + 1.25t^2) mV$