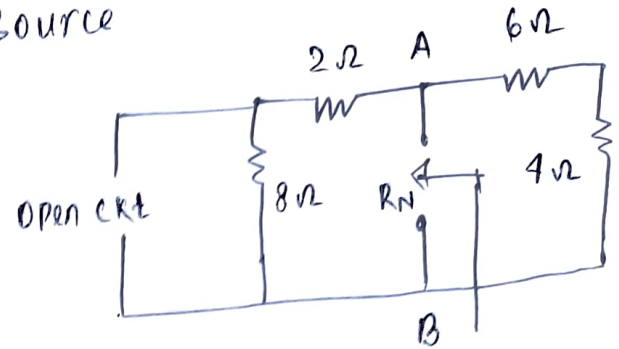


1. Step 1. Find Norton Resistance (R_N) $\rightarrow$ We need to remove the load resistance across ~~load~~ A-B terminal and deactivate the current source


$$R_N = (10\Omega) \parallel (10\Omega)$$

$$R_N = \frac{10 \times 10}{10 + 10} = 5\Omega$$



Step 2 Find Norton current (I_N) $\rightarrow$ short circuit the A-B terminal

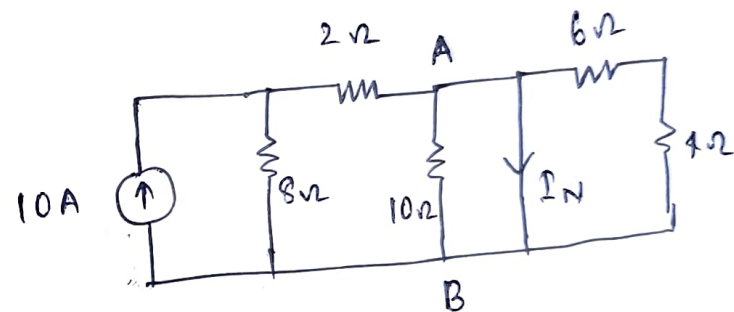so, no current will flow across 10Ω resistor, 6Ω resistor & 4Ω resistor




so, I_N will be same as current flowing 2Ω resistor

Using current divider rule, current through 2Ω resistor is $\frac{10 \times 8}{8 + 2} = 8A$

Step 3 Draw the equivalent Norton circuit and find out current value across load

Use current divider Rule

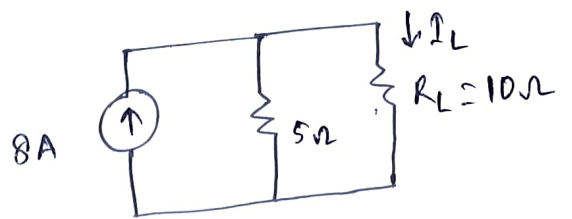
$$I_L = \frac{8 \times 5}{5 + 10} = \frac{8}{3} \text{ A}$$



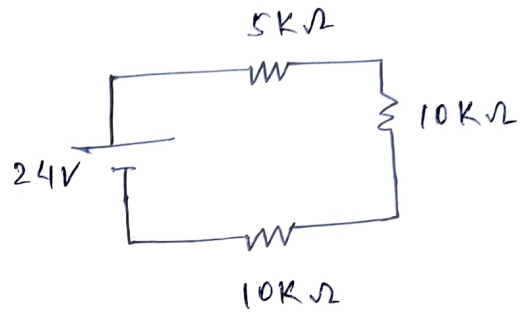Q. 2. Using voltage divider Rule

Voltage across $10\text{K}\Omega$ is

$$\frac{24 \times 10}{5 + 10 + 10} = 9.6\text{V}$$




Q. 3

Given $V_{in} = 50\text{V}$

$V_{out} = 20\text{V}$

$R_1 = 15\Omega$

$R_2 = ?$

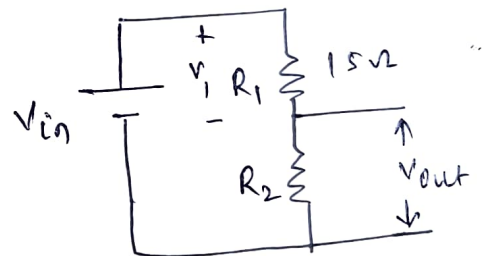

So, $V_{in} = V_1 + V_{out}$

$$50 = V_1 + 20$$

$$V_1 = 30\text{V}$$

$$\text{current through } R_1 = \frac{V_1}{R_1} = \frac{30}{15} = 2\text{A}$$

R_1 and R_2 are connected in series, so, current

through $R_2 = 2\text{A}$

$$\text{So, } R_2 = \frac{V_{out}}{2} = \frac{20}{2} = 10\Omega$$



Q. 4. (a)

Under steady state

current in $C_1 = 0$

current in $R_1 = 0$

voltage across $C_1 = V$

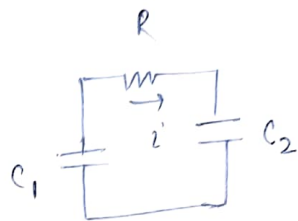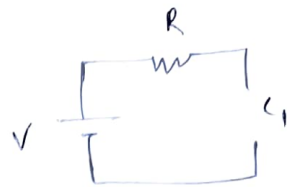

$$(b) \quad V_{C_1} = Ri + V_{C_2}$$

$$\Rightarrow V_{C_1} - Ri - V_{C_2} = 0 \quad \text{--- (A)}$$

$$\text{so, } i = C_2 \frac{dV_{C_2}}{dt} \quad \text{--- (B)}$$

$$\text{or } i = -C_1 \frac{dV_{C_1}}{dt} \quad \text{--- (C)}$$

so, Differentiating eqⁿ (A)

$$\frac{dV_{C_1}}{dt} - R \frac{di}{dt} - \frac{dV_{C_2}}{dt} = 0$$

$$-\frac{i}{C_1} - R \frac{di}{dt} - \frac{i}{C_2} = 0$$

$$\text{so, } \boxed{i \left(\frac{1}{C_1} + \frac{1}{C_2} \right) + R \frac{di}{dt} = 0}$$

$$(c) \quad \text{If } C_1 = C_2 = C$$

$$\text{then } R \frac{di}{dt} + \frac{2i}{C} = 0$$

$$R \frac{di}{dt} = -\frac{2i}{C}$$

$$\text{so, } \int \frac{1}{i} di = \int -\frac{R}{Ri} dt$$

$$\ln i = -2t/Ri + \ln K$$

$$\ln \left[\frac{i'}{K} \right] = -\frac{2t}{RC}$$

$$\frac{i'}{K} = e^{-2t/RC}$$


$$i' = K e^{-2t/RC} \quad \text{--- (D)}$$

Also, $i' = \frac{V_{C1} - V_{C2}}{R}$

at $t = 0^+$, $V_{C2} = 0$ (capacitor opposes sudden change in voltage)

so, $i' = \frac{V_{C1}}{R} = \frac{V}{R}$

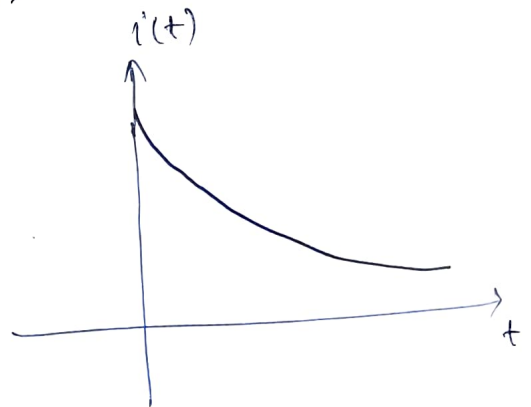so, (D) $\Rightarrow$ $i' = \frac{V}{R} e^{-2t/RC} \quad t > 0$




⑤

Step 1


Draw the circuit when the switch was at position 1. (Inductor will become short circuit in steady state on DC supply)

$$i_0 = \frac{V}{R_1}$$

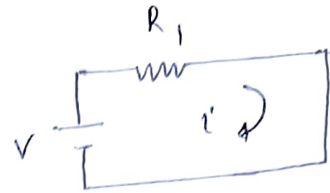

Step 2

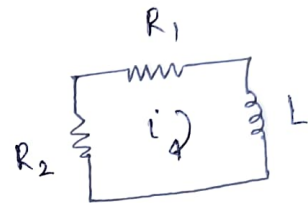Draw the circuit when switch is at position 2



Step 3

find τ

$$\tau = \frac{L}{R_1 + R_2}$$

Step 4

Write down current expression

$$i = i_0 e^{-t/\tau}$$


$$i = \frac{V}{R_1} e^{-(R_1 + R_2)t/L}$$

6. (a) Draw the equivalent circuit

$$R_{eq} = R_1 + R_2 = (1+2) = 3\Omega$$


$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = 2\mu F$$
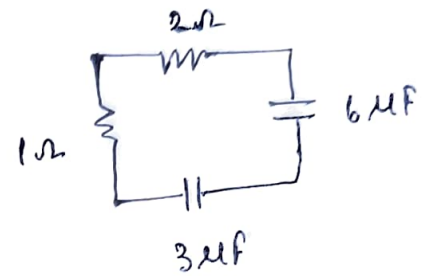
$$\tau = RC = (3 \times 2)\mu s = 6\mu s$$



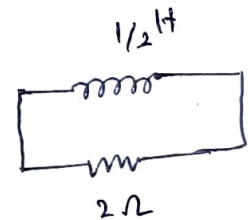(b) Draw the equivalent circuit

$$\tau = L/R = \frac{1}{2 \times 2} = 0.25 \text{ sec}$$




⑦

Step 1

Find the initial current through inductor when switch was closed (inductor will become short circuit in DC steady state)


$$i = \frac{120}{40} = 3 \text{ A}$$

$$i_L = \frac{120}{20} = 6 \text{ A}$$

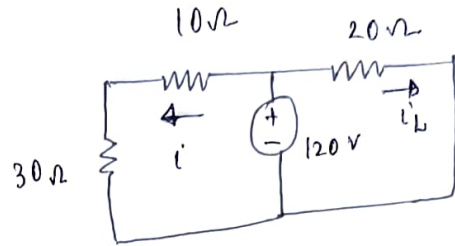

Step 2

Draw the circuit once switch is open

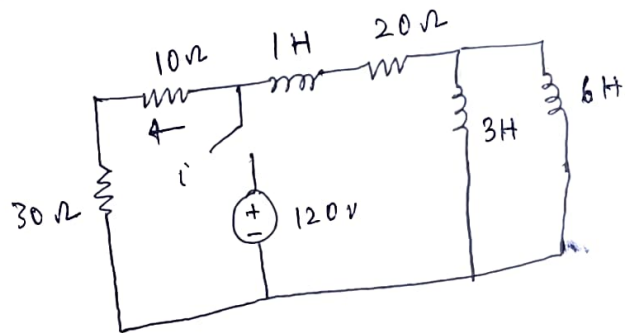

Step 3


Find out τ

$$\tau = \frac{L_{eq}}{R_{eq}}$$

$$L_{eq} = 1 + (3 || 6) = 3 \text{ H}$$

$$R_{eq} = (20 + 10 + 30) \Omega = 60 \Omega$$
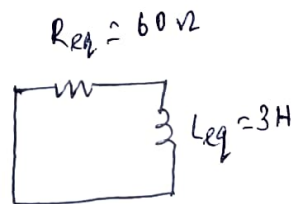
$$\tau = \frac{3}{60} = \frac{1}{20} \text{ sec}$$



Step 4

Write down current expression


$$i = 6e^{-t/\tau} = 6e^{-20t}$$

But given i is in opposite direction of calculated initial current

so

$$i = -1 = -6e^{-20t} \text{ A}$$

$t > 0$

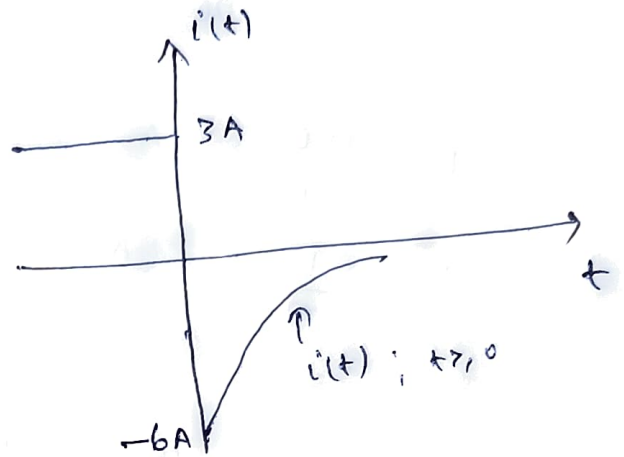

Q. Ans (a) We know that current through inductor can be written as

$$I = I_0 e^{-t/\tau} \quad \text{--- (1)}$$



$$R = 10 \Omega \text{ (Given)}$$

$$P_1 = I_1^2 R$$

$$P_2 = I_2^2 R$$

$$\frac{P_1}{P_2} = \frac{I_1^2}{I_2^2}$$

$$P_2 = 0.5 P_1 \rightarrow \text{as per question}$$

$$\text{so, } I_2 = \sqrt{0.5} I_1$$

$$\text{so, (i) } \Rightarrow \sqrt{0.5} I_1 = I_1 e^{-t/\tau}$$

$$\ln(\sqrt{0.5}) = -t/\tau$$

$$t/\tau = 0.347$$

$$\text{put } t = 1 \text{ sec (according to question)}$$

$$\text{so, } \frac{1}{\tau} = 0.347 \Rightarrow \tau = 2.88 \text{ s}$$

$$\tau = \frac{1}{0.347}$$

$$\Rightarrow L = \frac{R}{0.347} = \frac{10}{0.347} = 28.82 \text{ H}$$

$$\frac{L}{R} = \frac{1}{0.347}$$

8. (b)

So, $\therefore$ 10H introduces 0.5Ω resistance



$$\therefore 1\text{H} \quad \therefore \quad \frac{0.5}{10} \Omega$$

$$\therefore L \quad \therefore \quad \frac{0.5L}{10} \Omega$$

$$\text{So, } R_{eq} = R_L + 10 = \left(\frac{0.5L}{10} + 10 \right) \Omega$$

So, we know that

$$\tau = \frac{L}{R_{eq}}$$

$$\tau = \frac{L}{\left(\frac{0.5L}{10} + 10 \right)}$$

$$\Rightarrow \tau = \frac{L \times 10}{0.5L + 100}$$

$$\Rightarrow \tau (0.5L + 100) = 10L$$

Put $\tau = 2.88 \text{ sec}$ from (a)

$$\boxed{L = 33.64 \text{ H}}$$


(9) since both wheels are same in appearance and dimension, they have similar mass and inertia. Still one wheel has a larger time constant (twice), this is because it has lesser friction compared to wheel. Therefore, it will be easier to pedal. So, the wheel with larger time constant will be easier to pedal.

10

step 1

form the ckt before switch was open

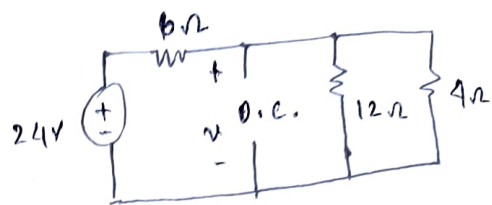The capacitor will be open circuit in steady state for DC supply




$$\text{voltage across capacitor } V_c = \frac{24 \times (12 || 4)}{(12 || 4) + 6}$$

as 12Ω and 4Ω are connected in parallel and their equivalent will be 3Ω

$$\text{so, } V_c = \frac{24 \times 3}{3 + 6} = 8V = V_0$$

step 2

draw the ckt after switch is open

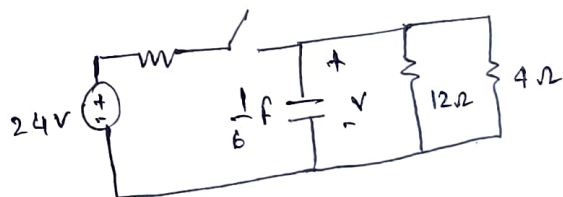

step 3

find out τ

$$\tau = R_{eq} \times C$$

R_{eq} across C will be $(12 || 4)\Omega = 3\Omega$

$$\text{so } \tau = 3 \times \frac{1}{6} = 0.5 \text{ sec}$$

step 4

write the voltage expression across capacitor

$$V_c(t) = V_0 e^{-t/\tau}$$


$$V_c(t) = 8e^{-2t}$$

$t \geq 0$

⑪ step 1 Find the initial current through inductor when switch was closed (inductor will be short circuit in steady state for DC supply)

Apply nodal analysis at V
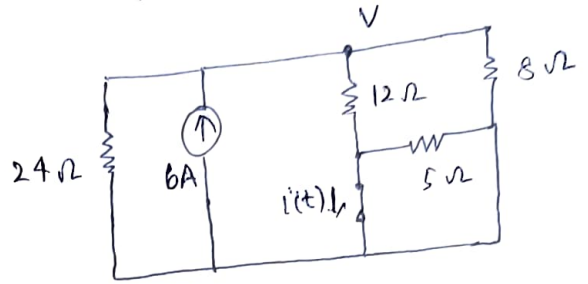
$$-6 + \frac{V}{24} + \frac{V}{12} + \frac{V}{8} = 0 \quad \text{--- (1)}$$




There will be no current through 5Ω resistor as it is short circuit

so, solve eqⁿ (1) $\Rightarrow V = 24V$

so, current through inductor will be $\frac{V}{12} = 2A$

step 2

Draw the circuit once switch is open

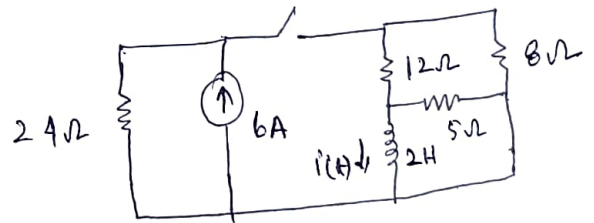

step 3

find out τ

$$\tau = L/R$$

$$R_{eq} = (12+8) \parallel 5 = 4\Omega$$

$$\text{so, } \tau = \frac{2}{4} = 0.5 \text{ sec}$$

Step 4

Write down current expression through inductor

$$i(t) = i_0 e^{-t/\tau}$$

$$\boxed{i(t) = 2e^{-2t}} \quad t \geq 0$$