

1. a) heating load = 5 kW

motor load = 50 kVA at 0.6 pf (lag) = 30 kW + j40 kVAR

so, Total load = 35 kW + j40 kVAR

$$S = VI^*$$

$$I = \left( \frac{S}{V} \right)^* = \left[ \left( \frac{35 + j40}{240} \right) \times 10^3 \right]^*$$


$$I = 221.46 \angle -48.81^\circ \text{ A}$$

⑥ plant power factor =  $\cos(48.81)_{\text{lag}} = 0.66 \text{ lag}$

⑦ Now, improved power factor = 0.95 lag

$$\text{i.e. } \phi = \cos^{-1}(0.95) = 18.19^\circ$$

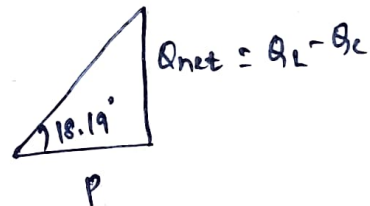
$$\text{so, } \tan(18.19^\circ) = \frac{Q_L - Q_C}{P}$$



$$0.329 = \frac{Q_L - Q_C}{35 \text{ kW}}$$

$$0.329 = \frac{40 - Q_C}{35 \text{ kW}}$$

$$Q_C = 28.5 \text{ kVAR}$$

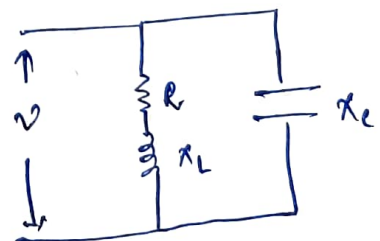

$$\text{so, } \frac{V^2}{X_C} = Q_C$$

$$\text{on calculation } C = 1.57 \text{ mF}$$

$$\text{Put } \omega = 100 \pi \text{ rad/s}$$

① so, Net power Demand =  $P_{net} + jQ_{net}$

$$= 35 \text{ kW} + j(40 - 28.5) \text{ kVAR}$$

$$= 35 \text{ kW} + j11.5 \text{ kVAR}$$

$$I = \left( \frac{P}{V} \right)^* = \left[ \left( \frac{35 + j11.5}{240} \right) \times 1000 \right]^*$$

$$I = 153.5 \angle -18.18^\circ \text{ A}$$

② yes, addition of capacitor in parallel to R-L load improves the power factor and thus reduces the overall demand of current.

② Given  $C = 0.5 \mu\text{F}$   
 coil  $\rightarrow R = 40 \Omega$ ,  $L = 0.32 \text{ H}$

$$R_c = 20 \Omega$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = 2500 \text{ rad/s}$$

$$f_0 = \frac{\omega_0}{2\pi} = 397.89 \text{ Hz}$$

$$X_L = j\omega L = j800 \Omega$$

$$X_C = \frac{-j}{\omega C} = -j800 \Omega$$
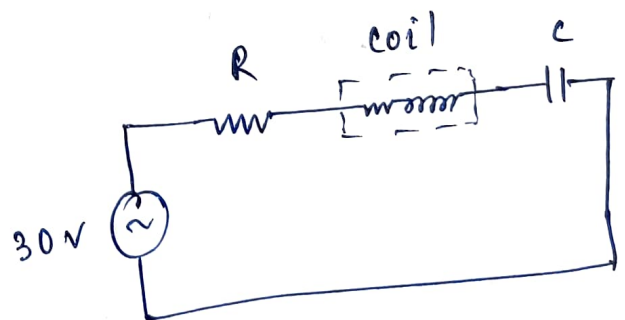
$$I_0 (\text{at resonance}) = \frac{V}{R_{net}} = \frac{30}{60} \text{ A} = 0.5 \text{ A}$$



so,

a) voltage across  $20\Omega$  resistor  $i_s = 0.5 \times 20 = 10\text{ V}$

voltage across capacitor  $= I_0 X_C = 400 \angle -90^\circ \text{ V}$

voltage across coil  $= I_0 (40 + j800) = 400.5 \angle 87.14^\circ \text{ V}$

(b) current  $= \frac{V}{R + jX_{\text{net}}} = \frac{30}{60 + j0} = 0.5 \text{ A}$

(c)  $P = I^2 R_{\text{net}} = (0.5)^2 (40 + 20) = 15 \text{ W}$

(3)


Given

$$R = 10\Omega$$

$$L = 30\text{ mH}$$

$$C = 1\mu\text{F}$$

$$V = 10\text{ V}$$

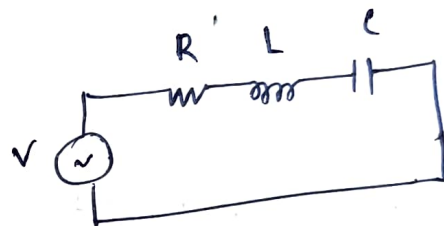

Frequency at which voltage developed across capacitor is max<sup>m</sup> can be found by  $\frac{dV_C}{df} = 0$

so,

$$f_c = f_0 \sqrt{1 - \frac{R^2 C}{2L}} \quad \text{--- (1)}$$

where  $f_c \rightarrow$  frequency at which  $V_C$  is max<sup>m</sup>

$f_0 \rightarrow$  resonant frequency

$$\text{so, } f_0 = \frac{1}{2\pi\sqrt{LC}} = 918.88 \text{ Hz}$$

(1)  $\Rightarrow$   $f_c = 918.11 \text{ Hz}$

so, at  $f_c$

$$X_L = j \times 2\pi \times f_c \times L = j 173.06 \Omega$$

$$X_C = \frac{-j}{2\pi \times f_c \times C} = -j 173.35 \Omega$$

$$I \text{ at } f_c = \frac{10}{\sqrt{R^2 + (X_{net})^2}} = 1.167 \text{ A}$$

$$\text{so, } \boxed{V_C = I X_C = 173.35 \angle -88.33^\circ \text{ V}}$$

④ dial setting 80 means 800 kHz

$$\text{so, } f_0 = 800 \text{ kHz}$$

$$f_0 = \frac{1}{2\pi \sqrt{LC}}$$

$$L = \frac{1}{4\pi^2 C \times f_0^2} \quad \left[ \text{put } C = 10 \text{ f} \right]$$

$$\boxed{L = 39.6 \mu\text{H}}$$

⑤  $R = 10\Omega$ ,  $L = 159\mu H$ ,  $V = 50mV$ ,  $f_{supplied} = 1MHz$

①  $C = \frac{1}{4\pi^2 \times L \times f_0^2}$  (at resonance)  
take  $f_0 = f_{supplied}$

so,  $C = 159.8 \text{ pF}$

② current at resonance ( $I_0$ ) =  $\frac{V}{R} = \frac{0.05}{10} = 5mA$

Now,  $A/q$ ,

$0.1 \times I_0 = \frac{5}{\sqrt{10^2 + X_{net}^2}}$

$0.5 = \frac{50}{\sqrt{10^2 + X_{net}^2}}$

(where  $X_{net} = X_L - X_C$ )

so,  $0.5 = \frac{50}{\sqrt{10^2 + (X_L - X_C)^2}}$

$X_L - X_C = 99.5$  — (i)


$X_L = j \times 2\pi \times f_0 \times 159 \times 10^{-6} = 999.03\Omega$

$X_C = \frac{-j}{2\pi \times f_0 \times C}$  — (ii)

so, from

(i) & (ii)  $\Rightarrow$

$C = 176.93 \text{ pF}$

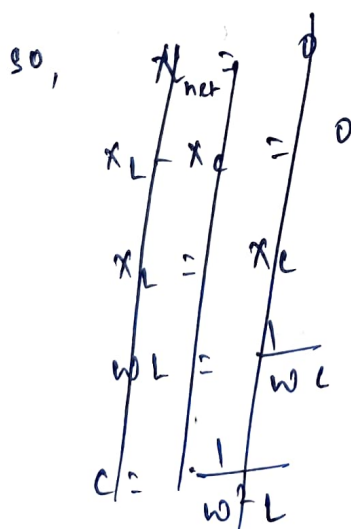

⑥ Given  $R = 5\Omega$ ,  $L = 4\text{mH}$ ,  $C = 0.1\mu\text{F}$

max<sup>m</sup> rms current flows when circuit is at resonant condition

$$I_{0,\text{rms(max)}} = \frac{V_{\text{rms}}}{R} = \frac{10}{5} = 2\text{ A}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 7957.74\text{ Hz}$$

For a series RLC circuit at resonant cond<sup>n</sup>

$$Q = \frac{1}{R} \sqrt{L/C} = 40$$

$$|V_C| = |V_L| = QV = 400\text{ V}$$

⑦ Given series RLC ckt at resonant cond<sup>n</sup>

$$C = \frac{1}{4\pi^2 \times L \times f_0^2}$$

$$\left[ \begin{array}{l} f_0 = 800\text{ kHz} \\ L = 40\mu\text{H} \\ R = 4.02\Omega \end{array} \right]$$

$$C = 989.46\text{ pF}$$

$$\text{B.W.} = \frac{R}{L} = 100.5\text{ rad/s}$$

8. (a)

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$R = 4\Omega, L = 25\text{mH}, Q = 50$$

so,  $\boxed{Q = \frac{1}{R} \sqrt{\frac{L}{C}}}$

$$\boxed{C = 0.625 \mu\text{F}}$$

(b)  $\omega_1, \omega_2 = \mp \frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$   $\rightarrow \mp \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$

so,  $\boxed{\omega_1, \omega_2 = 7920 \text{ rad/s}, 8080 \text{ rad/s}}$  respectively

$$\boxed{\text{B.W.} = \omega_2 - \omega_1 = \frac{R}{L} = 160 \text{ rad/s}}$$

(c) at  $\omega_r$ , current flowing in series RLC ckt is  $\frac{V}{R}$

so,  $I_0 \text{ at } \omega_r = \frac{100}{4} = 25 \text{ A}$

so,  $\boxed{P_{\text{avg}} \text{ at } \omega_r = I_0^2 \times R = 25^2 \times 4 = 2500 \text{ W}}$

we know that at cut-off frequencies i.e. at  $\omega_1$  &  $\omega_2$ ,  $P_{\text{avg}}$  is half of  $P_{\text{avg}}$  is at  $\omega_r$

so,  $\boxed{P_{\text{avg}} \text{ at } \omega_1 \text{ \& } \omega_2 = \frac{P_{\text{avg}} \text{ at } \omega_r}{2} = 1250 \text{ W}}$



⑨ The tuner circuit is parallel RLC circuit. When the circuit operates at resonant cond<sup>n</sup>, it catches the selected frequency.

so,  $C = \frac{1}{4\pi^2 \times L \times f_0^2}$  — ①

considering high end of FM band,  $f_0 = 108 \text{ MHz}$

$L = 4 \mu\text{H}$  (Given)

so, ①  $\Rightarrow C = 0.543 \text{ pF}$

considering low end of FM band,  $f_0 = 88 \text{ MHz}$

①  $\Rightarrow C = 0.818 \text{ pF}$

so, range of variable capacitor to cover the entire band is from  $0.543 \text{ pF}$  to  $0.818 \text{ pF}$ .