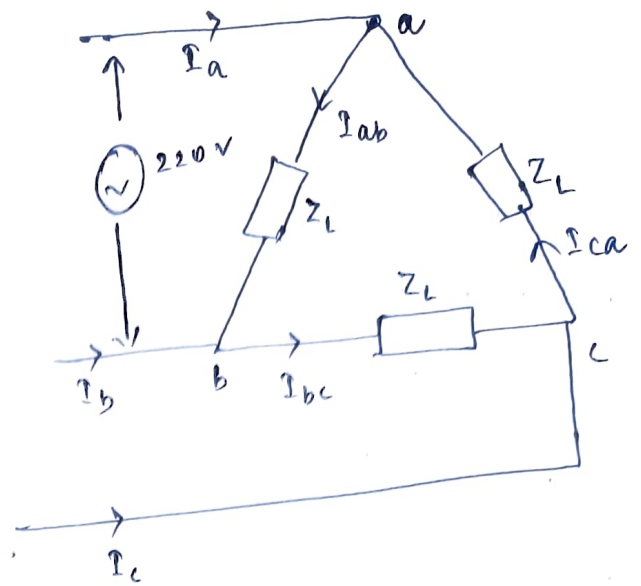


① Given $V_{L-L} = 220\text{ V}$

in Δ connected load,

$$V_L = V_{ph}$$



Phase currents :-

$$I_{ab} = \frac{V_{ab}}{Z_L} = \frac{220 \angle 0}{10 \angle -45^\circ} = 22 \angle 45^\circ \text{ A}$$

$$\text{H}, I_{bc} = \frac{V_{bc}}{Z_L} = \frac{220 \angle -120}{10 \angle -45^\circ} = 22 \angle -75^\circ \text{ A}$$

$$I_{ca} = \frac{V_{ca}}{Z_L} = \frac{220 \angle 120}{10 \angle -45^\circ} = 22 \angle 165^\circ \text{ A}$$

Line current

in Δ -connection,

$$I_L = \sqrt{3} I_{ph} \angle -30^\circ$$

$$\text{SO, } I_a = \sqrt{3} I_{ab} (\angle -30^\circ) = 38.105 \angle 15^\circ \text{ A}$$

$$\text{H}, I_b = \sqrt{3} I_{bc} (\angle -30^\circ) = 38.105 \angle -105^\circ \text{ A}$$

$$I_c = \sqrt{3} I_{ca} (\angle -30^\circ) = 38.105 \angle 135^\circ \text{ A}$$

②


Given

$$V_1 = 240 \angle 90^\circ \text{ V}$$

$$V_2 = 240 \angle -30^\circ \text{ V}$$

$$V_3 = 240 \angle -150^\circ \text{ V}$$

$$Z = 40 \angle -30^\circ \Omega$$

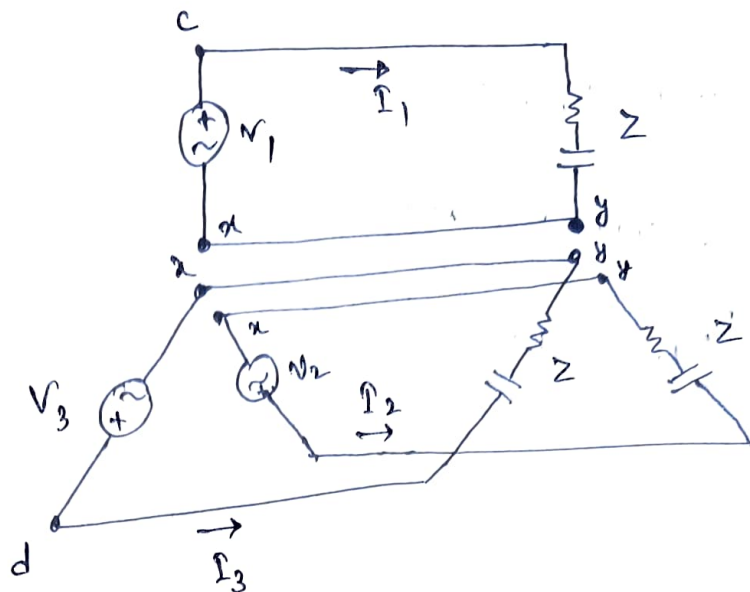

①
$$I_1 = \frac{V_1}{Z} = \frac{240 \angle 90^\circ}{40 \angle -30^\circ} \text{ A} = 6 \angle 120^\circ \text{ A}$$

$$I_2 = \frac{V_2}{Z} = \frac{240 \angle -30^\circ}{40 \angle -30^\circ} = 6 \text{ A}$$

$$I_3 = \frac{V_3}{Z} = \frac{240 \angle -150^\circ}{40 \angle -30^\circ} = 6 \angle -120^\circ \text{ A}$$

② If terminals x are connected together & y are connected together

$$I_{yx} = I_1 + I_2 + I_3$$


$$\text{so, } I_{yx} = 6 \angle 120^\circ + 6 + 6 \angle -120^\circ$$

$$I_{yx} = 0$$

$$\textcircled{c} \quad V_{cd} = V_1 - V_3 = (240 \angle 90^\circ) - (240 \angle -150^\circ)$$

$$\text{so, } \boxed{V_{cd} = 415.69 \angle 60^\circ \text{ V}}$$

$\textcircled{d}$

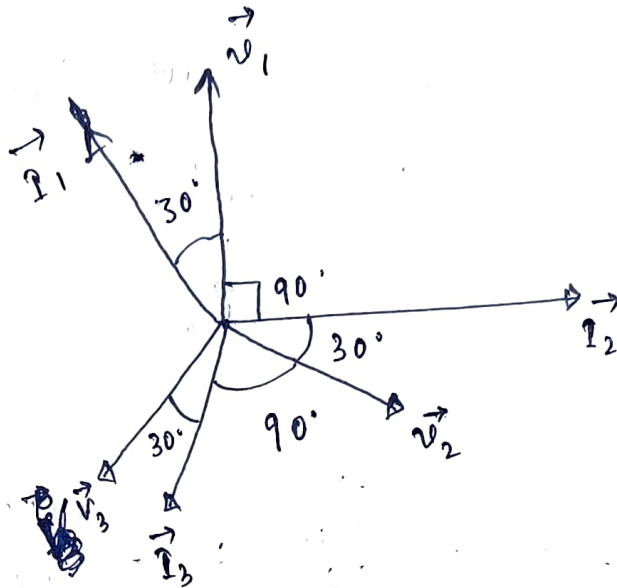


Given

$$\textcircled{3} \quad V_{ab} = 240 \angle 60^\circ \text{ V}$$

$$\text{so, } V_{bc} = 240 \angle -60^\circ \text{ V}$$

$$V_{ca} = 240 \angle -180^\circ \text{ V}$$

or, $240 \angle 180^\circ \text{ V}$

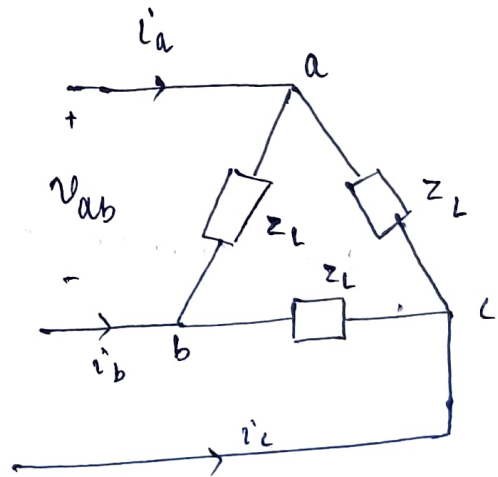


as, if we consider inductive ^{or capacitive} load, then phase angle of phase current would not exceed than $\pm 90^\circ$ to its corresponding phase voltage

$$\text{so, } I_{ca} = 6 \angle 200^\circ \text{ A}$$

$$I_{ab} = 6 \angle 80^\circ \text{ A}$$

$$I_{bc} = 6 \angle -40^\circ \text{ A}$$

Phasor diagram

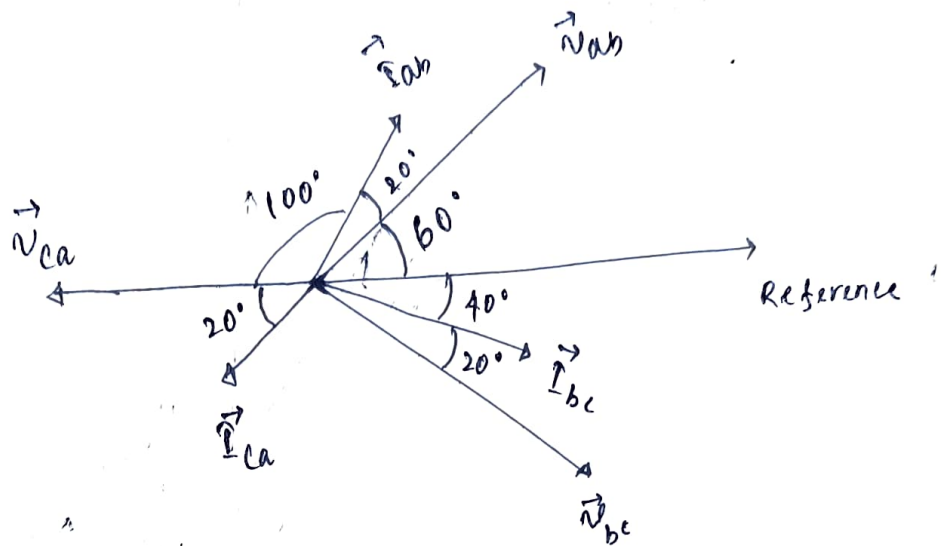

$$\textcircled{b} \quad Z_{ab} = Z_L = \frac{\vec{V}_{ab}}{\vec{I}_{ab}} = \frac{240 \angle 60^\circ}{6 \angle 80^\circ} = 40 \angle -20^\circ \Omega$$

$$= (37.59 - j13.68) \Omega$$

$\textcircled{2}$

$\textcircled{c}$

$$\boxed{\text{Line current} = \sqrt{3} \times \text{Phase current} \times (\angle -30^\circ)}$$

for Δ -connection

$$\text{so, } I_a = \sqrt{3} \times I_{ab} \times \angle -30^\circ = 10.39 \angle 50^\circ \text{ A}$$

$$\text{Hence, } I_b = I_a \angle -120^\circ = 10.39 \angle -70^\circ \text{ A}$$


$$I_c = I_b \angle -120^\circ = 10.39 \angle -190^\circ \text{ A}$$

④ (a) $Z_L = 20 \angle -30^\circ \Omega$

$V_{ab} = 240 \text{ V}$

$V_{bc} = 240 \angle -120^\circ \text{ V}$

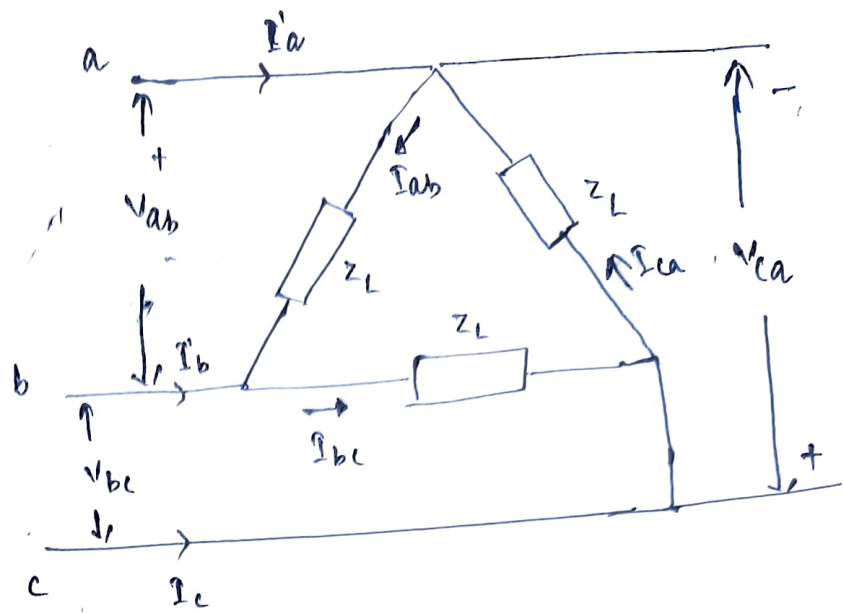$V_{ca} = 240 \angle -240^\circ \text{ V}$



⑤ In Δ connection ; $V_{ph} = V_{line}$

Phase currents

$$I_{ab} = \frac{V_{ab}}{Z_L} = \frac{240}{20 \angle -30^\circ} = 12 \angle 30^\circ \text{ A}$$

∴ $I_{bc} = I_{ab} \angle -120^\circ = \frac{V_{bc}}{Z_L} = 12 \angle -90^\circ \text{ A}$

$I_{ca} = I_{bc} \angle -120^\circ = I_{ab} \angle 120^\circ = \frac{V_{ca}}{Z_L} = 12 \angle 150^\circ \text{ A}$

Line currents

for Δ connection, $I_{line} = \sqrt{3} I_{ph} (\angle -30^\circ)$


∴ $I_a = \sqrt{3} \times I_{ab} \angle -30^\circ = 20.78 \text{ A}$

$I_b = I_a \angle -120^\circ = \sqrt{3} \times I_{bc} \angle -30^\circ = 20.78 \angle -120^\circ \text{ A}$

$I_c = I_a \angle 120^\circ = I_b \angle -120^\circ = \sqrt{3} \times I_{ca} \angle -30^\circ = 20.78 \angle 120^\circ \text{ A}$

©

Phasor Diagram

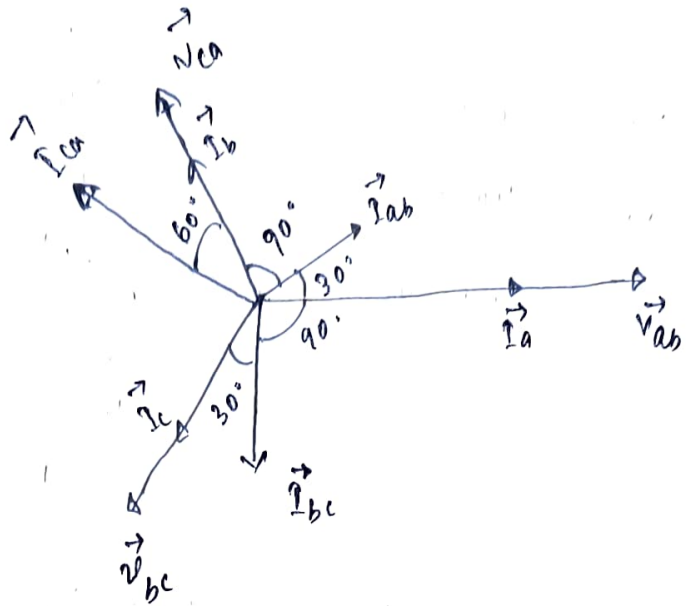


④ Total power = $3 V_{ph} I_{ph} \cos \phi$
 $= 3 \times 240 \times 12 \times \cos 30^\circ = 7.48 \text{ kW}$

⑤ Phase currents :-

$$I_{AB} = \frac{V_{ab}}{30 + j10} = \frac{173}{30 + j10}$$
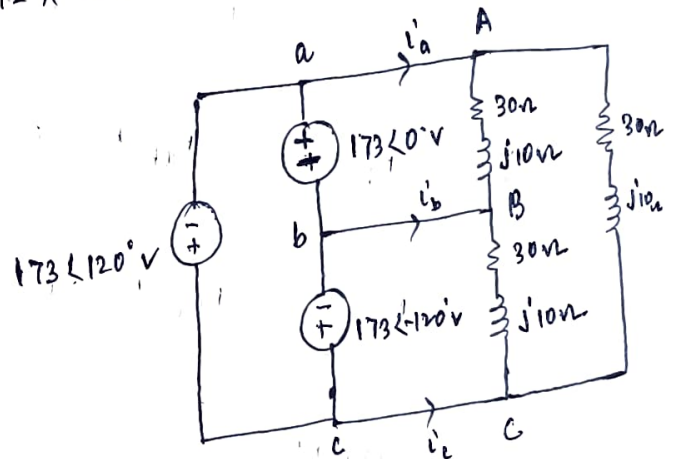
$$I_{AB} = 5.47 \angle -18.43^\circ \text{ A}$$



118, $I_{BC} = \frac{V_{bc}}{30 + j10} = 5.47 \angle -138.43^\circ \text{ A}$

$$I_{CA} = \frac{V_{ca}}{30 + j10} = 5.47 \angle 101.57^\circ \text{ A}$$

Line currents :-


In Δ connection : $I_L = \sqrt{3} I_{ph} \angle -30^\circ$

So, $I_a = 9.47 \angle -48.43^\circ \text{ A}$

$I_b = 9.47 \angle -168.43^\circ \text{ A}$

$I_c = 9.47 \angle 71.57^\circ \text{ A}$

⑥ Given $Z_L = (6 + j4) \Omega$

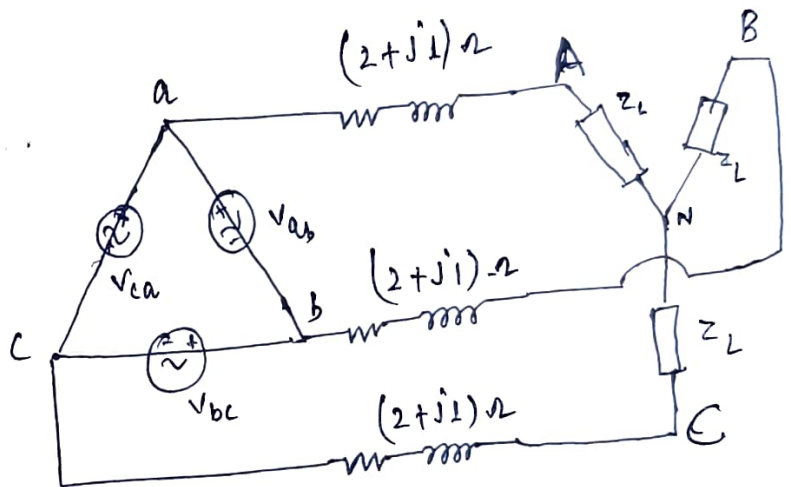

~~$V_{AN} = \frac{V_{ab} \angle -30^\circ}{\sqrt{3}}$~~ ~~$= \frac{12.73 \angle -62.005^\circ}{\sqrt{3}}$~~

$I_{AN} = \frac{V_{ab} \angle -30^\circ}{\sqrt{3} (8 + j5)} = 12.73 \angle -62.005^\circ \text{ A}$


$V_{ph, load} = I_{AN} \times Z_L = 91.79 \angle -28.31^\circ \text{ V}$

$V_{line, load} = V_{ph} \times \sqrt{3} \times \angle 30^\circ$

So, $V_{line, load} = 158.99 \angle 1.68^\circ \text{ V}$

7

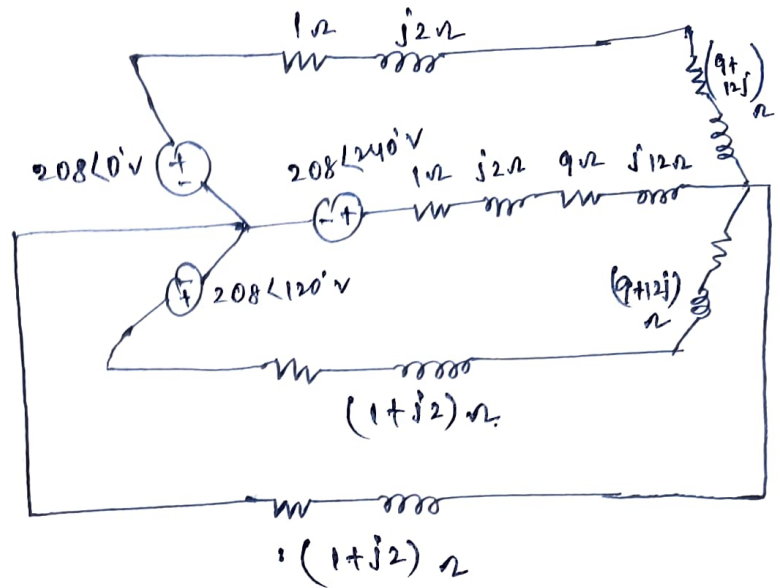Given configuration is
star connected load with
star connected source



so,

$$I_{\text{phase}} = I_{\text{line}} = \frac{V_{\text{phase}}}{\text{line impedance} + \text{load impedance}}$$

$$I_{\text{ph}} = \frac{208 \angle 0}{10 + j14} = 12.09 \angle -54.46^\circ \text{ A}$$

$$V_{\text{load, ph}} = Z_{\text{load}} \times I_{\text{ph}} = (9 + j12) (12.09 \angle -54.46^\circ) \text{ V}$$

$$V_{\text{load, ph}} = 181.35 \angle -1.33^\circ \text{ V}$$

$$\text{complex power } (S)_{\text{load}} = 3 V_{\text{ph, load}} \times I_{\text{ph}}^*$$

$$S_{\text{load}} = (3946.55 + j5262.05) \text{ VA}$$