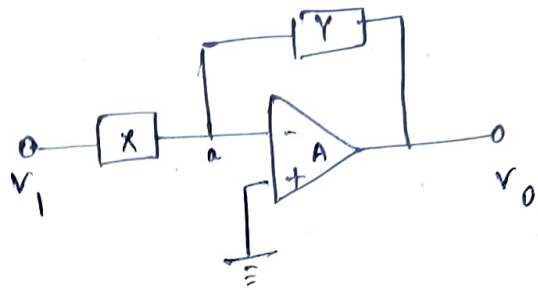


①

Given $X = L = (sL \text{ in } \Omega)$

$Y = R$



$\Rightarrow$ Applying virtual ground concept $\Rightarrow V_a = 0$

Nodal at point 'a'

$$\frac{V_a - V_1}{sL} + \frac{V_a - V_0}{R} = 0$$

$$\Rightarrow -\frac{V_1}{sL} - \frac{V_0}{R} = 0$$


$$\Rightarrow \boxed{\frac{V_0}{V_1} = -\frac{R}{sL} \text{ (in frequency domain)}}$$

$$\Rightarrow \boxed{V_0 = -\frac{R}{L} \int V_1 dt \text{ (in time domain)}}$$

$\Rightarrow$ The ckt performs integration operation.

② Since opamp is

ideal so, $V_x = V_y$

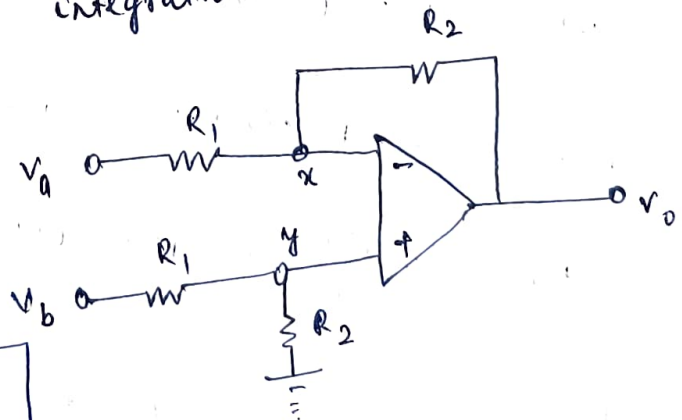

$$\boxed{V_y = V_b \frac{R_2}{R_1 + R_2} = V_x}$$

Now, applying nodal analysis at x

$$\frac{V_x - V_a}{R_1} + \frac{V_x - V_o}{R_2} = 0$$

$$\text{Put } V_x = V_b \frac{R_2}{R_2 + R_1}$$

$$\text{we get, } \boxed{V_o = \frac{R_2}{R_1} (V_b - V_a)} \quad \text{--- (A)}$$

(b) voltage subtraction

$$(c) \quad R_1 = R_2 = 50 \text{ k}\Omega, \quad V_a = -3 + \sin \omega t, \quad V_b = \sin \omega t + 2 \sin \omega t$$

$$\text{so, (A) } \Rightarrow \boxed{V_o = 3 + 2 \sin \omega t}$$

$$(3) \quad \text{Given } \text{S.R.} = 0.5 \text{ V}/\mu\text{s}, \quad f = 3000 \text{ Hz}, \quad \text{max}^m \text{ o/p} = 12 \text{ V (Peak)}$$

$$\text{Let } V_o = 12 \sin \omega t \quad \text{where } \omega = 2\pi \times 3000 = 6000\pi \text{ rad/s}$$

$$\text{S.R.} = \frac{dV_o}{dt} = 12\omega \cos \omega t$$


$$\left| \frac{dV_o}{dt} \right| = 12 \times 6000\pi = 0.226 \text{ V}/\mu\text{s}$$

as calculated S.R. is less than given S.R. (0.5 V/ μ s)
so, opamp can handle its o/p without slew. Slew will not happen.

4)

Since the opamp is ideal,

$$V_b = V_a = 2V$$

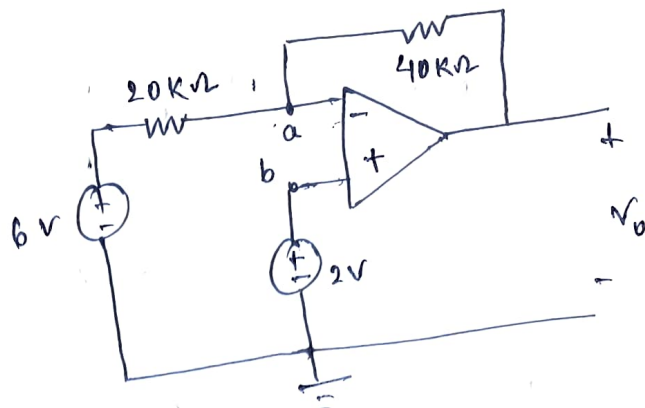


apply nodal analysis at a

$$\frac{V_a - 6}{20k\Omega} + \frac{V_a - V_o}{40k\Omega} = 0$$

$$\Rightarrow V_o = -6V$$

5)

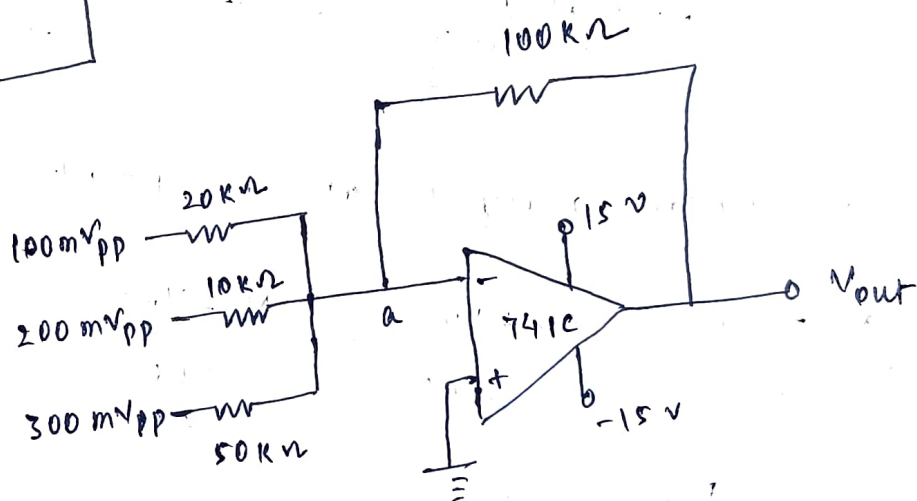

$$V_a = 0 \text{ (virtual ground)}$$

apply nodal analysis at V_a

$$\text{We get } V_{out} = -5 \times 0.1V_{pp} - 10 \times 0.2V_{pp} - 2 \times 0.3V_{pp}$$

$$V_{out} = -3.1V_{pp}$$

so,

$$V_{out} = 3.1V \text{ (Peak to Peak)}$$

since $V_{out} < V_{saturation}$

⑥ Slew Rate = $\frac{\text{change in o/p voltage}}{\text{time duration}}$


$$S.R. = \frac{0.25}{0.1} \text{ V/}\mu\text{s}$$

$$S.R. = 2.5 \text{ V/}\mu\text{s}$$

⑦

⑧ Given $V_a = 4\text{V}$

$V_x = 0$ [virtual ground concept]

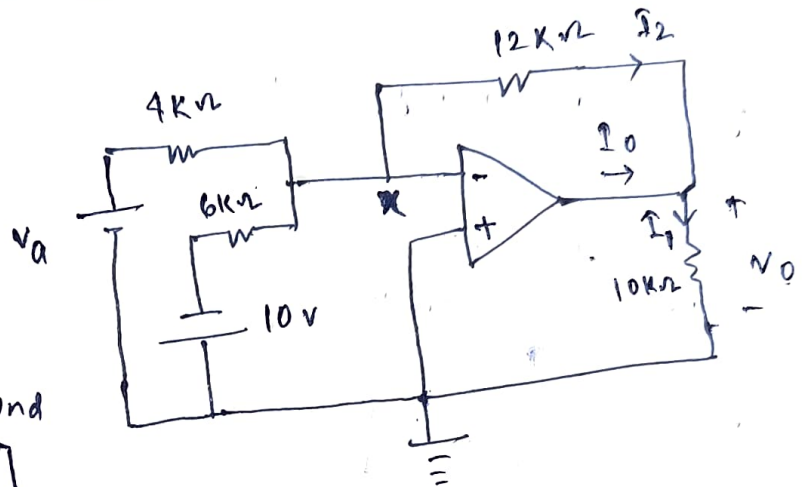

apply nodal analysis at a point

$$\frac{V_a - V_x}{4000} + \frac{V_x + 10}{6000} + \frac{V_x - V_o}{12000} = 0$$

$$V_o = 8\text{V}$$

Now, $I_o = I_1 - I_2$ — (A)

$$I_1 = \frac{V_o}{10\text{k}\Omega} = 0.8 \text{ mA}$$

$$I_2 = \frac{-8}{12\text{k}\Omega} = -0.67 \text{ mA}$$

so, (A) $\Rightarrow I_o = 1.47 \text{ mA}$

⑤ once again, writing nodal analysis equation at x ($v_x = 0$)

$$-\frac{v_a}{4000} + \frac{10}{6000} = \frac{v_o}{12000}$$

$$\boxed{v_o = -3v_a + 20}$$

①

to operate in linear region, $v_o < v_{\text{saturation}}$

$$\text{i.e. } -12 < v_o < 12 \text{ (volt)}$$

case 1

when $v_o > 12$

$$\text{①} \Rightarrow -3v_a + 20 > 12$$

$$\boxed{v_a < \frac{32}{3} \text{ V}}$$

case 2

when $v_o < 12$

$$\text{①} \Rightarrow -3v_a + 20 < 12$$


$$\boxed{v_a > \frac{8}{3} \text{ V}}$$

so, from case 1 & case 2

$$\boxed{\frac{8}{3} < v_a < \frac{32}{3} \text{ (volt)}}$$

$\Rightarrow$ range of v_a
for linear operation

8

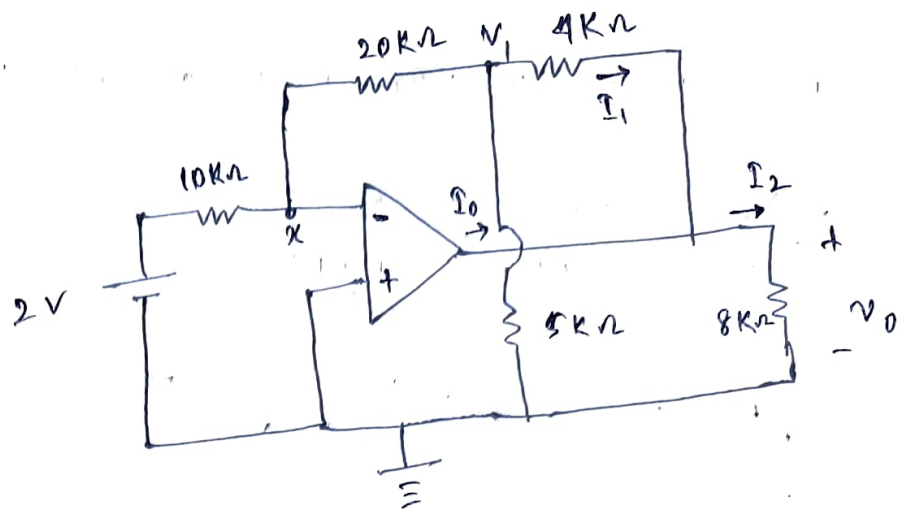

$V_x = 0$ (virtual ground)

Writing nodal equations at node x

$$\frac{V_x - 2}{10000} + \frac{V_x - V_1}{20000} = 0$$

$$\boxed{V_1 = -4V}$$

Writing nodal equation at node V_1

$$\frac{V_1}{5000} + \frac{V_1 - V_x}{20000} + \frac{V_1 - V_0}{4000} = 0$$

$$\boxed{V_0 = -8V}$$


So, $I_0 = I_2 - I_1$ — (A)

$$I_2 = \frac{V_0}{8k\Omega} = -1mA$$

$$I_1 = \frac{V_1 - V_0}{4k\Omega} = 1mA$$

(A) $\Rightarrow \boxed{I_0 = -2mA}$

9

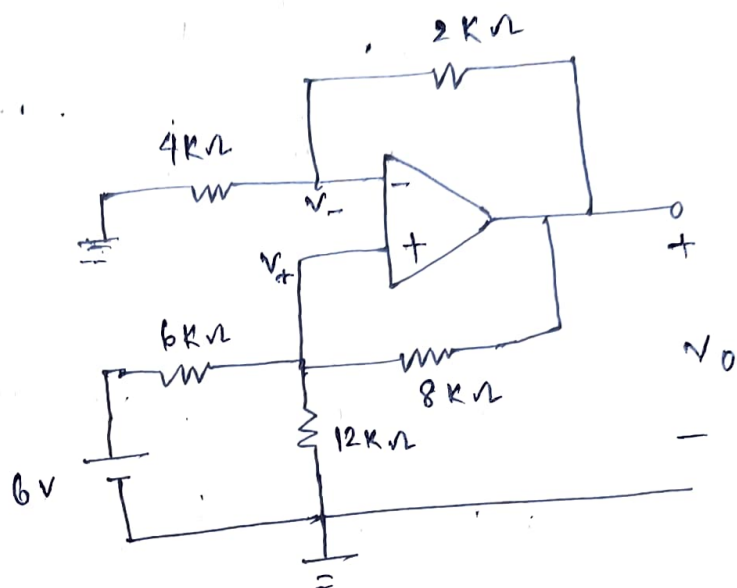

Writing nodal analysis equation at V_+

$$\frac{V_+}{12000} + \frac{V_+ - 6}{6000} + \frac{V_o - V_o}{8000} = 0 \quad \text{--- (1)}$$

Also, $V_+ = V_-$ [virtual ground]

Writing nodal eqⁿ at V_-


$$\frac{V_- - 0}{4000} + \frac{V_- - V_o}{2000} = 0 \quad \text{--- (2)}$$

Solve eqⁿ (1) & (2)

$$V_- = V_+ = \frac{2V_o}{3}$$

$$\therefore \boxed{V_o = 8V}$$

(10)

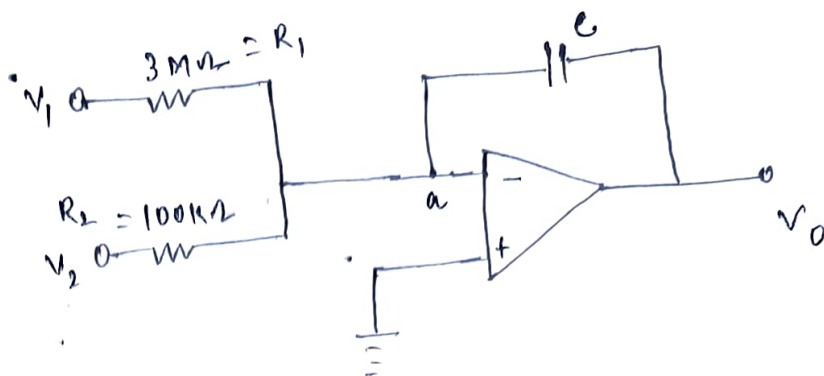

$$R_1 = 3\text{ M}\Omega, \quad R_2 = 100\text{ k}\Omega, \quad C = 2\text{ }\mu\text{F}$$

$$V_1 = 100 \cos 2t \text{ mV}, \quad V_2 = 0.5 t \text{ mV}$$

Now, $V_a = 0$ [virtual ground]

Writing nodal eqⁿ at node 'a' in s-domain

$$-\frac{V_1}{R_1} - \frac{V_2}{R_2} - V_0 \cdot sC = 0$$

$$\Rightarrow V_0 = -\frac{1}{R_1 R_2 C s} [V_1 R_2 + V_2 R_1]$$

in time domain

$$\Rightarrow V_0 = -\frac{1}{R_1 R_2 C} \left[\int_0^t V_1 R_2 dt + \int_0^t V_2 R_1 dt \right]$$

Putting all values , we get

$$V_0 = -\frac{1}{R_1 R_2 C} \left[\frac{10^{-2}}{2} R_2 \sin 2t + 0.25 \times 10^{-3} R_1 t^2 \right]$$

$$V_0 = - (83.3 \sin 2t + 1.25 t^2) \text{ mV}$$